3

3.31

Answer
$$\checkmark$$

$$\begin{bmatrix}
7 & -3 & -2 \\
-3 & 9 & -6 \\
-2 & -6 & 12
\end{bmatrix}
\begin{bmatrix}
I_1 \\
-4 \\
I_3
\end{bmatrix} = \begin{bmatrix}
-48 \\
V_2 \\
48
\end{bmatrix}$$

$$I = \begin{bmatrix}
-42/5 \\
-4 \\
3/5
\end{bmatrix}$$

With I_1 as the left loop, I_2 as the top loop, and I_3 as the right loop, all clockwise.

$$P = V(I_3 - I_1)$$

= -432 W

3.41

$$egin{bmatrix} 7 & -2 & -4 \ -2 & 8 & -6 \ -4 & -6 & 15 \end{bmatrix} egin{bmatrix} I_1 \ I_2 \ 2 \end{bmatrix} = egin{bmatrix} 0 \ -6 \ V_3 \end{bmatrix} \ I = egin{bmatrix} 19/13 \ 29/26 \ 2 \end{bmatrix}$$

With I_1 as the outer loop, I_2 as the top loop, and I_3 as the right loop, all clockwise.

$$V = IR = I_1 = 19/13 \ V$$

3.47

$$\begin{bmatrix} 6 & 2 & 0 & 0 \\ 2 & 11 & -9 & -3 \\ 0 & -9 & 16 & 8 \\ 0 & -3 & 8 & 8 \end{bmatrix} \begin{bmatrix} I_x \\ 3I_x \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} v_x \\ v_x \\ 0 \\ -2 \end{bmatrix}$$

$$I = \begin{bmatrix} 6/49 \\ 18/49 \\ 103/196 \\ -125/196 \end{bmatrix}$$

With I_1 as the outer loop, I_2 as the left loop, and I_3 as the inner diamond loop, I_4 as the top of the inner diamond loop, all clockwise.

$$I_3 = 103/196 \ V$$

3.63

a

✓ Answer

$$egin{bmatrix} 1 & 1 & 1 & 0 \ -12 & 12 & 0 \ 0 & 0 & 30 \end{bmatrix} egin{bmatrix} 1 \ I_2 \ I_3 \end{bmatrix} = egin{bmatrix} v_1 \ 0 \ 0 \end{bmatrix} \ I = egin{bmatrix} 1 \ 1 \ 0 \ 0 \end{bmatrix}$$

With clockwise loops, from left to right.

$$V_x'=0$$

b

✓ Answer

$$\begin{bmatrix} 12 & 0 \\ 0 & 30 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -10 \\ 10 \end{bmatrix}$$

$$I = \begin{bmatrix} -5/6 \\ 1/3 \end{bmatrix}$$

With clockwise loops, from left to right.

$$V_x''=5~V$$

C

✓ Answer

$$egin{bmatrix} 12 & 0 & 0 \ 0 & 30 & -10 \ 0 & -10 & 31 \end{bmatrix} egin{bmatrix} I_2 \ I_3 \ -3 \end{bmatrix} = egin{bmatrix} 0 \ 0 \ v_2 \end{bmatrix} \ I = egin{bmatrix} 0 \ -1 \ -3 \end{bmatrix}$$

With clockwise loops, from left to right.

$$V_x^{\prime\prime\prime}=-15~V$$

d

✓ Answer

$$V_x = -10~V$$

3.68

$$\begin{bmatrix} 8 & -2 & -2 \\ -2 & 8 & -2 \\ -2 & -2 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 6 \\ -8 \\ -12 \end{bmatrix}$$

$$I = \begin{bmatrix} -1/10 \\ -3/2 \\ -19/10 \end{bmatrix}$$

With I_1 as the left loop, I_2 as the top loop, and I_3 as the right loop, all clockwise.

$$V_{Th}=4I_3=-rac{38}{5}~V$$

$$\begin{bmatrix} 8 & -2 & -2 & 0 \\ -2 & 8 & -2 & 0 \\ -2 & -2 & 8 & -4 \\ 0 & 0 & -4 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 6 \\ -8 \\ -12 \\ 0 \end{bmatrix}$$

$$I = \begin{bmatrix} -21/20 \\ -49/20 \\ -19/4 \\ -19/4 \end{bmatrix}$$

$$I = egin{bmatrix} -21/20 \ -49/20 \ -19/4 \ -19/4 \end{bmatrix}$$

$$R_{Th}=rac{V_{Th}}{I_4}=rac{8}{5}~\Omega$$

$$V_{Th}=-rac{38}{5}~V \ R_{Th}=rac{8}{5}~\Omega$$

$$R_{Th} = \frac{8}{5} \Omega$$

3