

PHYS115 PHYS121 PHYS123
PHYS116 PHYS122 PHYS124
Lab Cover Letter

Author (You) Trevor Signature: Trevor

I declare that this assignment is original and has not been submitted for assessment elsewhere, and acknowledge that the assessor of this assignment may, for the purpose of assessing this assignment: (1) reproduce this assignment and provide a copy to another member of faculty; and/or (2) communicate a copy of this assignment to a plagiarism checking service (which may then retain a copy of this assignment on its database for the purpose of future plagiarism checking).

Lab Partner(s) Lauren

Date Performed 05/09/2024 Date Submitted 05/09/2024

Lab (such as #1: UNC) #1-DLUR

TA: El

GRADE (to be filled in by your TA) See your TA for detailed feedback.
An 'x' next to a subcategory means you need to improve this aspect of your work.

Paper Subtotals (points)

- | | |
|--|--|
| <p>() General (6)
____ Sig. figs.
____ Units
____ Clarity of Presentation
____ Format</p> <p>() Abstract (4)
____ Quantity or principle
____ How measurement was made
____ Numerical Results
____ Conclusion</p> <p>() Intro & Theory (9)
____ Basic principle
____ Main equations to be used
____ Apparatus
____ What will be plotted
____ Fitting parameters related</p> <p>() Exp. Procedures (15)
____ Description
____ Stating and justifying uncertainties
____ Data Record
____ Quality of Lab Work</p> <p>() Analysis & Error Analysis (20)
____ Discussion
____ Equations & Calculations
____ Presentation inc. Graphs, Tables
____ Results Reported & Reasonable
____ Underlined items addressed</p> | <p>() Discussion & Conclusions (6)
____ Numerical comparison of results
____ Logical conclusions
____ Discussion of pos. errors
____ Suggestions to reduce errors</p> <p>() Paper Total (60 points)
(30 points for CME or EPF)</p> <p>() Notebook (10 points)
____ Format (<i>proper style, following directions</i>)
____ Apparatus (<i>brief description of equipment, including sketches</i>)
____ Data (<i>including computer file names and manually recorded data</i>)
____ Experimental Technique (<i>describing your procedures; stating & justifying uncerts.</i>)
____ Analysis (<i>results and errors</i>)</p> <p>() Worksheet(s)/Fill-in-the-Blank-Report (30 points) if applicable</p> <p>() Adjustments – late submissions, improper procedures, etc. – or bonus points for exceptional work.</p> <p>() Total Grade</p> <p>Graded by _____ (TA's initial)</p> |
|--|--|

PHYS 122-119B Lab 1: DC-CIR

Course & Section: PHYS 122-119B

Station 32

Section D: Ohm's Law

1.

DMM reading for the resistor

✓ Answer ✓

$$R = 99.5 \pm 0.1 \Omega$$

2.

List your data for minimum and maximum current, with error estimates. Don't forget units. Also, staple to this worksheet a copy of your plot, including the linear fit.

✓ Answer

$$I_{min} = 21.4 \pm 0.1 \text{ mA} \quad V = 2.118 \pm 0.001 \text{ V}$$

$$I_{max} = 26.5 \pm 0.1 \text{ mA} \quad V = 2.620 \pm 0.001 \text{ V}$$

3.

List your linear fit parameters, with error estimates from *Origin*

✓ Answer

$$\text{SLOPE: } 0.0984 \pm 0.0006 \frac{\text{V}}{\text{mA}}$$

$$\text{INTERCEPT: } 0.01 \pm 0.02 \text{ V}$$


4.

Comment on the comparison of the DMM value and Origin fit. (Use additional sheets if necessary)

✓ Answer

They are not particularly close, they are approximately 10SD away by the larger error, but I would trust the Origin result over the DMM as there is smaller error.

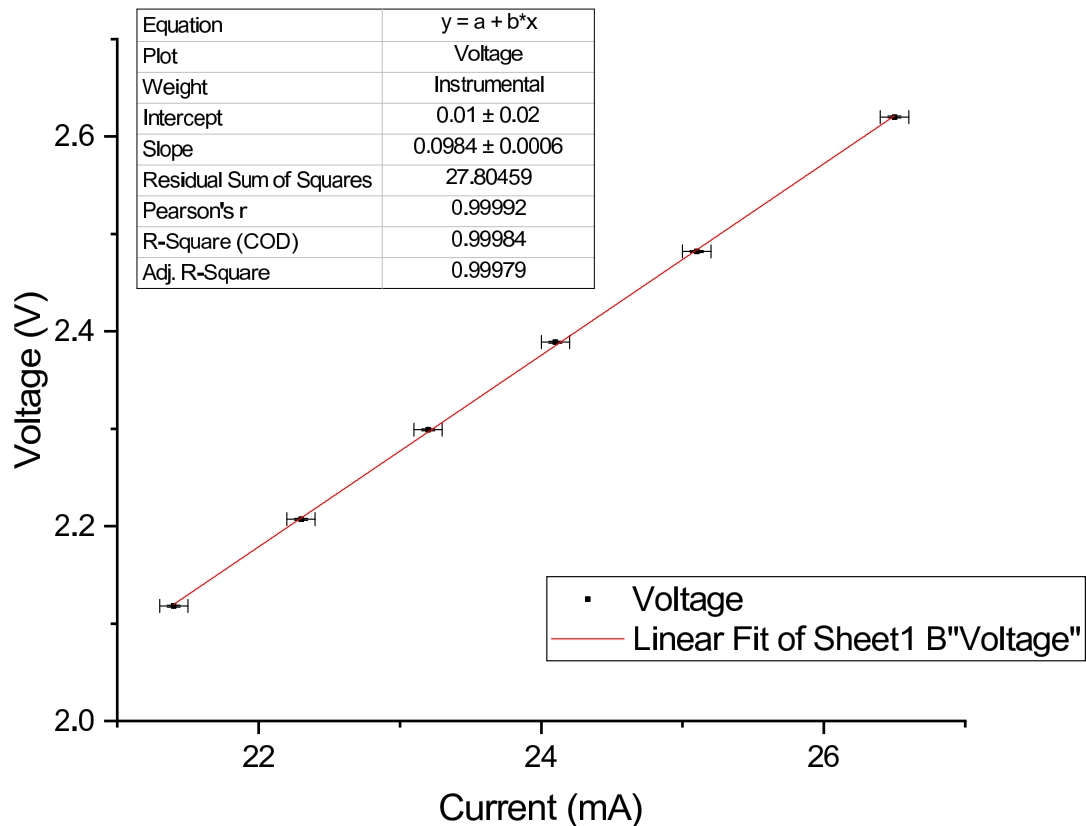Linear Fit of Voltage vs. Current in a 100Ω Resistor - Lauren and Trevor



Section E.1: Series Resistors

5.

Enter below the data (with error estimates) for series resistors.

✓ Answer

Resistor #	Resistance Ω	Theoretical Sum Ω	Voltage V ± 0.001	Current mA	Experimental Sum Ω
1	$99.5 \pm 0.1 \Omega$	99.5Ω	2.703	27.4 ± 0.01	98.65 ± 0.05
2	$98.8 \pm 0.1 \Omega$	198.3Ω	2.789	14.1 ± 0.01	197.8 ± 0.2
3	$0.99 \pm 0.01 \text{ k}\Omega$	1188.3Ω	2.866	2.239 ± 0.001	1280.0 ± 0.7
4	$47.1 \pm 0.1 \Omega$	1235.4Ω	2.867	2.161 ± 0.001	1326.7 ± 0.8

6.

Attach a sheet that describes in detail how you found the errors in each entry for two resistors in series. This should include errors in any raw data you took as well as error propagation through any equations that you used (see App. V of the lab manual)

✓ Answer

$$R = \frac{V}{I}$$

$$\delta_{RV} = \frac{1}{I}$$

$$\delta_{RI} = \frac{V}{I^2}$$

$$\delta_R = \sqrt{\left(\frac{\delta_V}{I}\right)^2 + \left(\frac{V\delta_I}{I^2}\right)^2}$$

□

7.

Compare the theory to the experiment. (Use additional sheets if necessary.)

✓ Answer

Our experimental sum was roughly in the same ballpark as the theoretical sum, but only within about 10SD of each other. I would say this is fairly bad, but they are relatively close in orders of magnitude.

Section E.2: Parallel Resistors

8.

Enter below the data from your table of part E.2 for parallel resistors.

✓ Answer

Resistor #	Resistance Ω	Theoretical Sum Ω	Voltage $V \pm 0.001$	Current $\text{mA} \pm 0.1$	Experimental Sum Ω
1	$99.5 \pm 0.1 \Omega$	99.5Ω	2.707	27.4	98.8 ± 0.4
2	$98.8 \pm 0.1 \Omega$	49.57Ω	2.548	51.7	49.3 ± 0.1
3	$0.99 \pm 0.01 \text{ k}\Omega$	47.21Ω	2.532	53.9	46.98 ± 0.09
4	$47.1 \pm 0.1 \Omega$	23.58Ω	2.259	96.4	23.43 ± 0.03

9.

Attach a sheet that describes in detail how you found the errors in each entry for 2 resistors in parallel.

✓ Answer

$$R = \frac{V}{I}$$

$$\delta_{RV} = \frac{1}{I}$$

$$\delta_{RI} = \frac{V}{I^2}$$

$$\delta_R = \sqrt{\left(\frac{\delta_V}{I}\right)^2 + \left(\frac{V\delta_I}{I^2}\right)^2}$$

□

10.

Compare the theory to the experiment. (Use additional sheets if necessary.)

✓ Answer

This time, my error was roughly within 4SD, which I would consider fairly close to the expected values.

Sections F & G: Where Ohm's Law Fails & Power Limits

11.

What resistance did you measure with the DMM?


✓ Answer

$$R = 1.7 \pm 0.1 \, \Omega$$

12.

Attach your Origin plot of R vs. I

✓ Answer

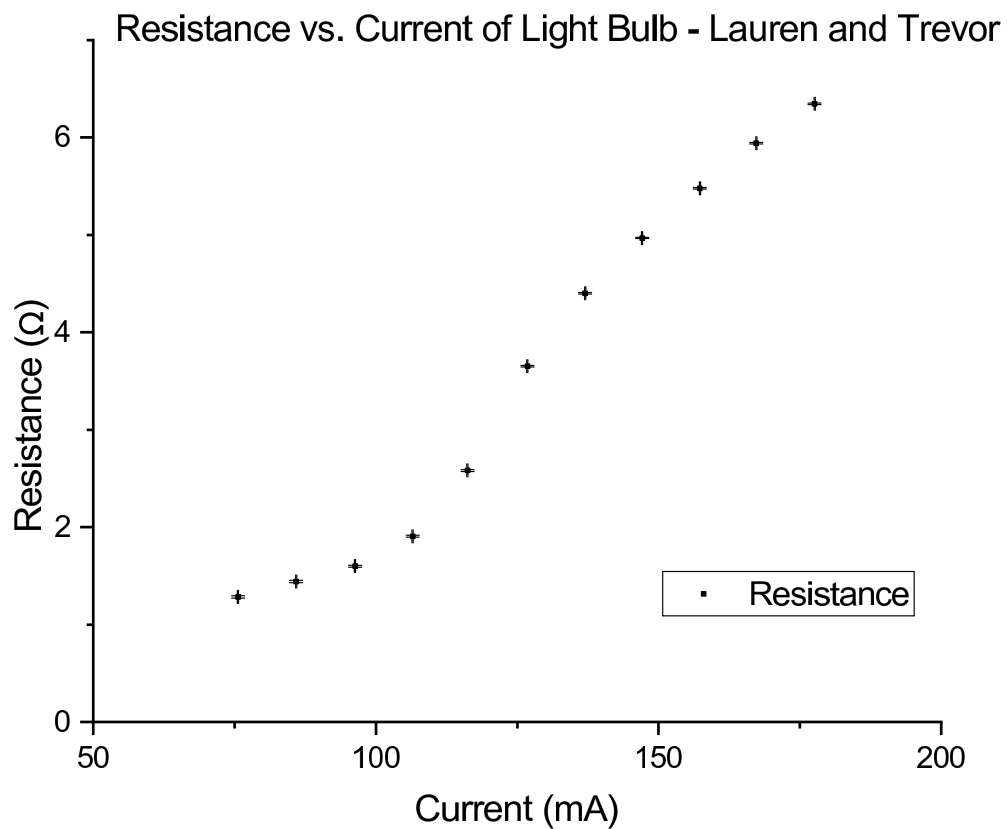

13.

Comment on Ohm's Law as it applies to the incandescent bulb and compare the DMM reading to the data in your plot: (Use additional sheets if necessary.)

✓ Answer

The resistance of the light bulb does not stay the same at around 1.7Ω , instead it non-linearly increases with the current. This is an unexpected result.

14.

What is the maximum rated voltage for a 100Ω , $\frac{1}{4}$ W resistor

✓ Answer

$$V = 5 \text{ V}$$

15.

What is your personal resistance?

✓ **Answer**

$$R = 0.130 \pm 0.001 \text{ M}\Omega$$

16.

What voltage across your hands would result in a power that could destroy a $100 \text{ }\Omega$, $\frac{1}{4} \text{ W}$ resistor?

✓ **Answer**


$$\frac{13000 \text{ }\Omega}{4 \text{ W}} = V^2$$
$$V = 180 \text{ V}$$

2

$$V = IR$$

$$P = IV = I^2 R = V^2 / R$$

DB-1

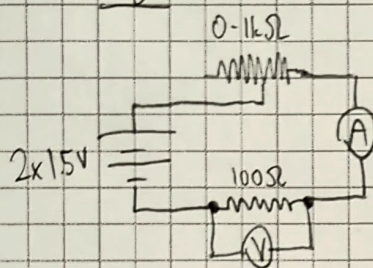

$$R = 99.5 \pm 0.1 \Omega$$

$$A = 26.5 \pm 0.1 \text{ mA}$$

$$V = 2.620 \pm 0.001 \text{ V}$$

$$A = 21.4 \pm 0.1 \text{ mA}$$

$$V = 2.118 \pm 0.001 \text{ V}$$

A (mA)	V (V)
21.4 ± 0.1	2.118 ± 0.001
22.3 ± 0.1	2.207 ± 0.001
23.2 ± 0.1	2.299 ± 0.001
24.1 ± 0.1	2.389 ± 0.001
25.1 ± 0.1	2.482 ± 0.001
26.5 ± 0.1	2.620 ± 0.001

E1

$$R_1 = 99.5 \pm 0.1 \Omega$$

$$R_2 = 98.8 \pm 0.1 \Omega$$


$$R_3 = 0.99 \pm 0.01 \text{ k}\Omega$$

$$R_4 = 47.1 \pm 0.01 \Omega$$


#	Theoretical (Ω)	± 0.001 V (V)	± 0.01 I (mA)	$R_{eq} (\Omega)$	$\delta R (\Omega)$
R_1	R_1 99.5	2.703	27.4	98.65	0.08 0.05
$R_{1,2}$	$R_1 + R_2$ 198.3	2.789	14.1	197.8	0.16
$R_{1,2,3}$	$R_1 + R_2 + R_3$ 1188.3	2.866	2.239 ± 0.001	1280.0	0.73
$R_{1,2,3,4}$	$R_1 + R_2 + R_3 + R_4$ 1235.4	2.867	2.239 2.161 ± 0.001	1326.7	0.77

$$R = \frac{V}{I}$$
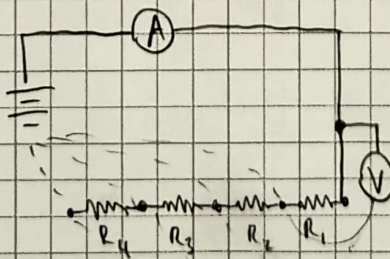
$$\delta R = \sqrt{\left(\frac{\delta V}{I}\right)^2 + \left(\frac{V \delta I}{I^2}\right)^2}$$



E2

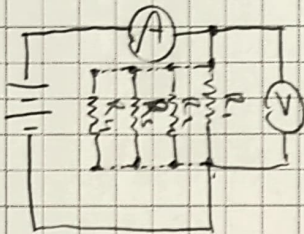

$$R_1 = 99.5 \pm 0.1 \, \Omega$$

$$R_2 = 98.8 \pm 0.1 \, \Omega$$

$$R_3 = 0.99 \pm 0.01 \, \text{k}\Omega$$

$$R_4 = 47.1 \pm 0.01 \, \Omega$$

#	(Ω) Theoretical	(V) V	(mA) I	(Ω) R_{eq}	(Ω) δ_R
R_1	99.5	2.707 ± 0.001	27.4 ± 0.1	98.8	0.36
R_2	49.57	2.548 ± 0.001	51.7 ± 0.1	49.28	0.077
$R_{1,2,3}$	47.21	2.532 ± 0.001	53.9 ± 0.1	46.98	0.089
$R_{1,2,3,4}$	23.58	2.259 ± 0.001	96.4 ± 0.1	23.43	0.026


$$R = \frac{V}{I}$$

$$\delta_R = \sqrt{\left(\frac{\delta V}{I}\right)^2 + \left(\frac{V \delta I}{I^2}\right)^2}$$

F

$$R = 1.7 \Omega$$

$$\pm 0.1$$

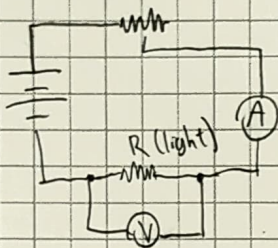

± 0.1 $I (mA)$	± 0.001 $V (V)$	$R_{eq} (\Omega)$
75.6	0.097	
177.6	1.127	
85.9	0.124	
96.3	0.154	
106.5	0.203	
116.2	0.300	
126.8	0.463	
137.0	0.603	
147.1	0.731	
157.3	0.862	
167.3	0.994	

G

$$P = 0.25 W$$

$$R = 100 \Omega$$

$$R = 0.130 M\Omega$$

$$\frac{100 \Omega}{4 W} = V^2$$

$$V = 5V$$

Rated at 25V

$$\frac{130,000 \Omega}{4 W} = V^2$$

$$V = 180V$$