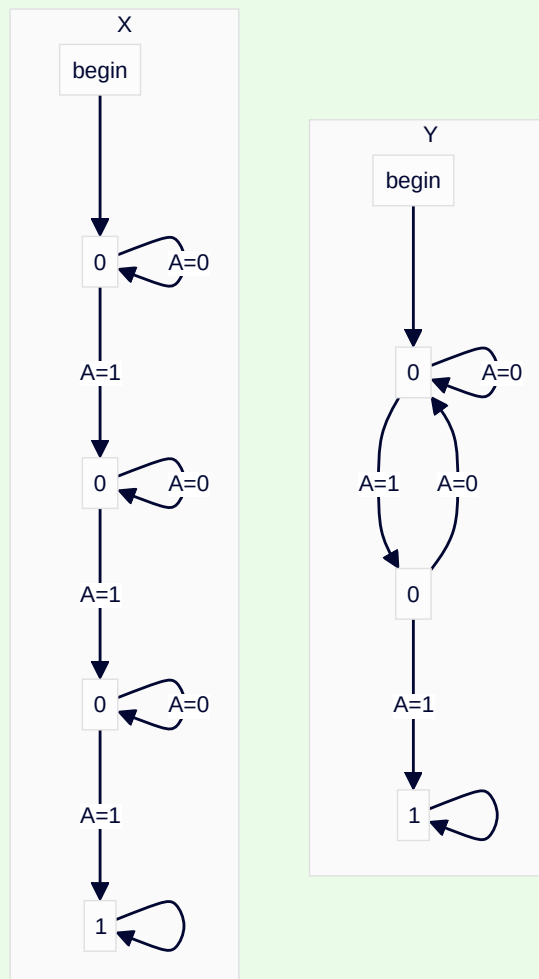


1

Draw the state diagram for the following problem: There is one input A and two outputs X and Y . X becomes 1 if A has been 1 for at least three cycles altogether (not necessarily consecutively). Y becomes 1 if A has been 1 for at least two consecutive cycles.

✓ Answer ✓



2




Given the following excitation and output equations, write the state transition and output tables. X is the input, Z is the output. Draw the sequential logic circuit. Please note that state memory is using positive-edge triggered D flip-flops.

$$D1 = Q1' + Q1 \cdot Q2$$


$$D2 = Q2' \cdot X'$$

$$Z = Q1' + Q2$$

✓ Answer

   

Q1	Q2	X	D1	D2	Z
0	0	0	1	1	1
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	1	0	1

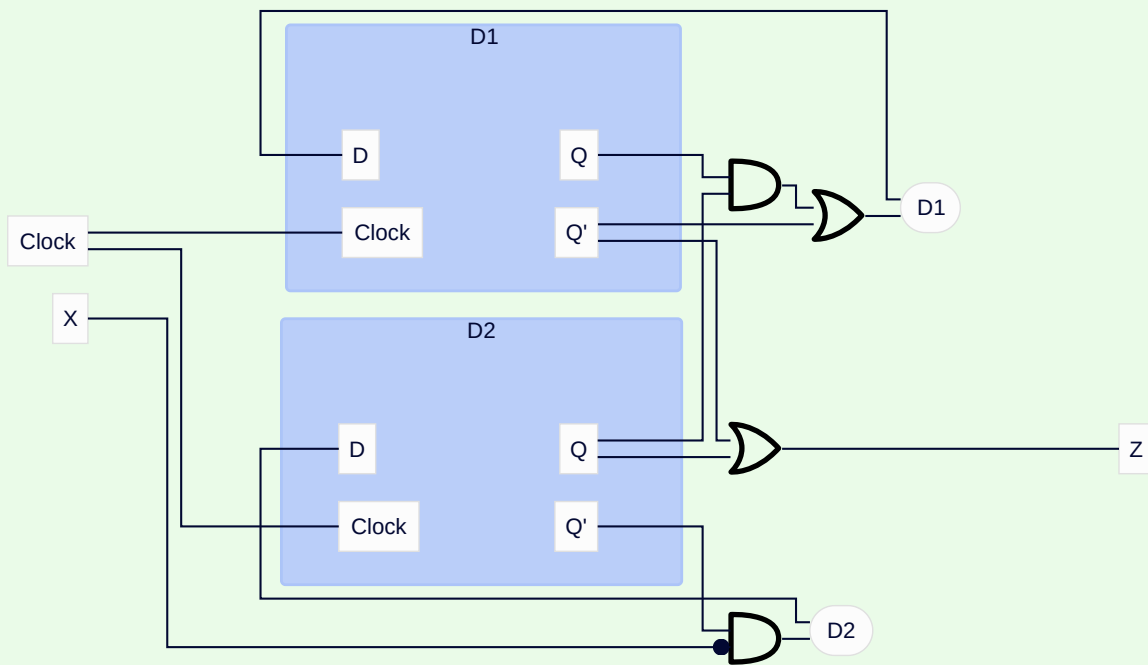

3


Design a 3-bit binary counter with counting sequence 0, 3, 4, 5, 6, 7, 0, 3, ...

The counter will increment at each clock tick. Use binary state assignments. Use D flip-flops, and combinational logic gates.

Follow the steps below:

1. Draw a state diagram.
2. Write a state transition table.
3. Write state transition, and excitation equations.
4. Draw the circuit.

✓ Answer

 


Y2	Y1	Y0	Y2*	Y1*	Y0*
0	0	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

$$D0 = Q0'$$

$$D1 = Q1' \cdot (Q2 \wedge Q0)' + Q1 \cdot Q0'$$

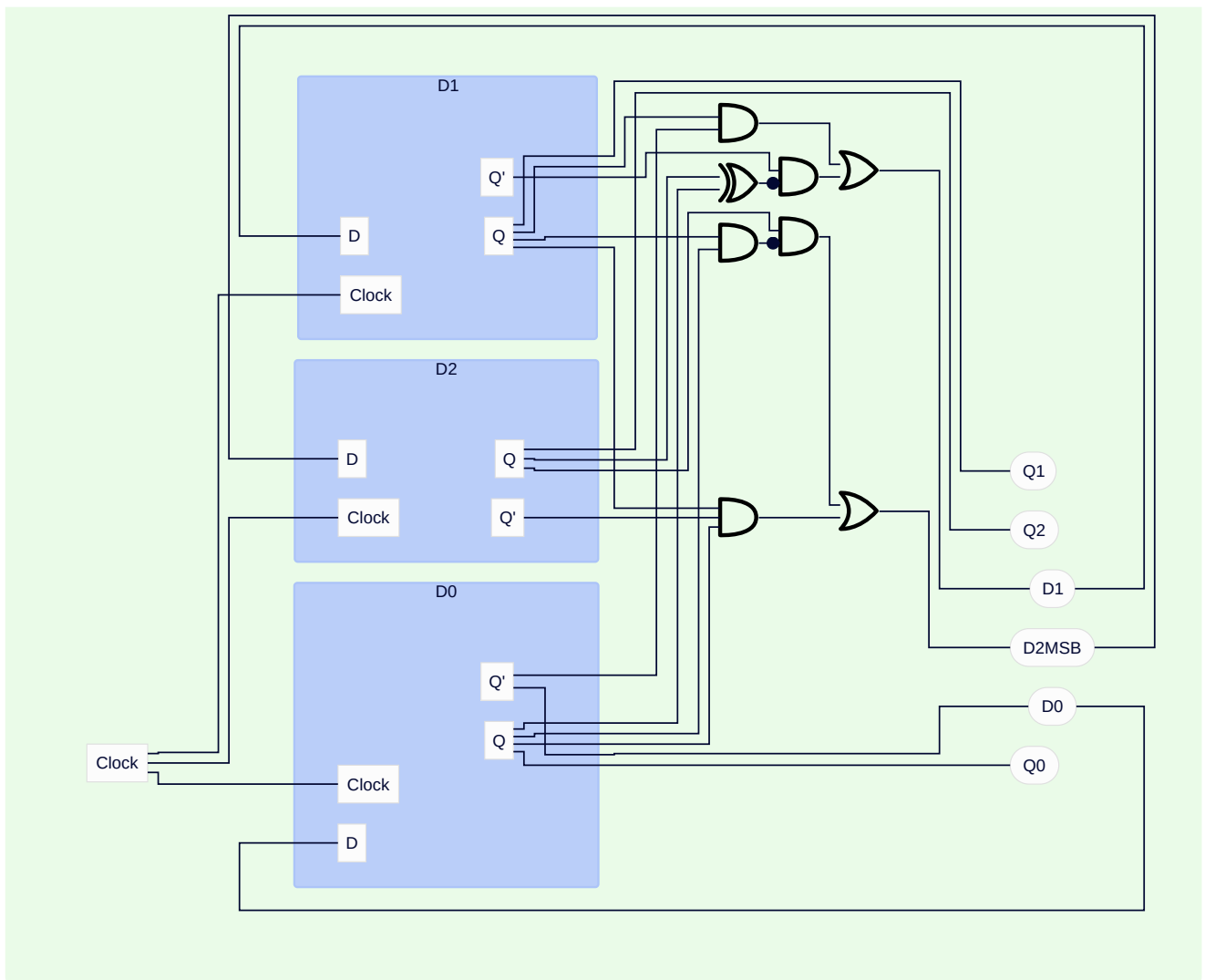
$$D2 = Q2' \cdot Q1 \cdot Q0 + Q2 \cdot (Q1 \cdot Q0)'$$



4

Design a 4-bit ripple up counter using only four D flip-flops.


✓ Answer

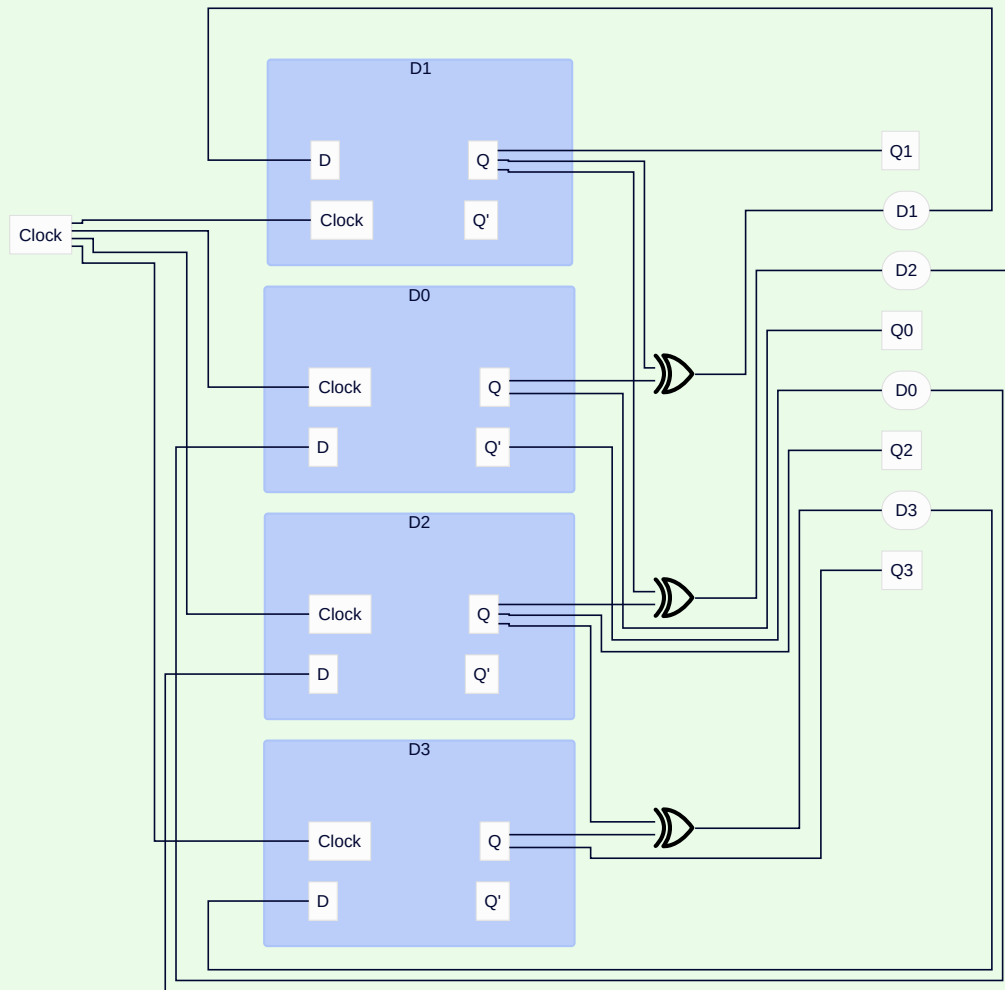

5

Using two 74x163 counters, design a counter with counting sequence 0, 128, 129,..., 254, 255, 0, 128, 129, ... , 254, 255. Logic 0 and 1 are available.


✓ Answer

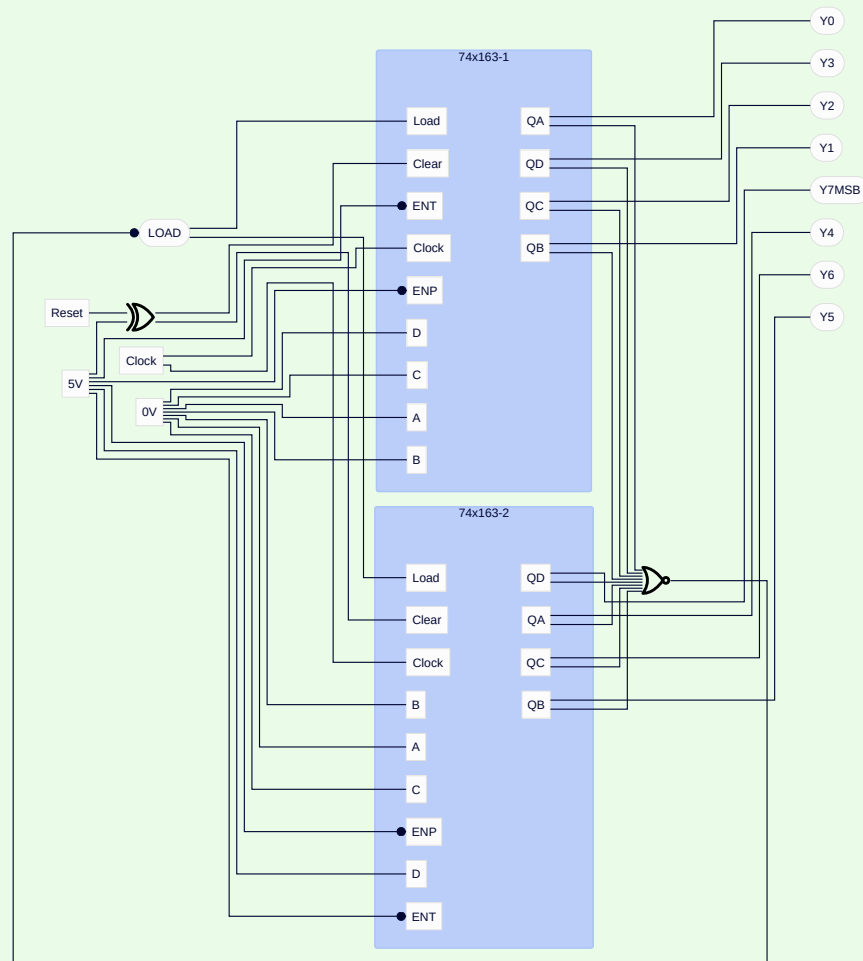

6

Using one 74x169 and three inverters, design a counter with the counting sequence 4, 3, 2, 1, 0, 11, 12, 13, 14, 15, 4, 3 ...

✓ Answer

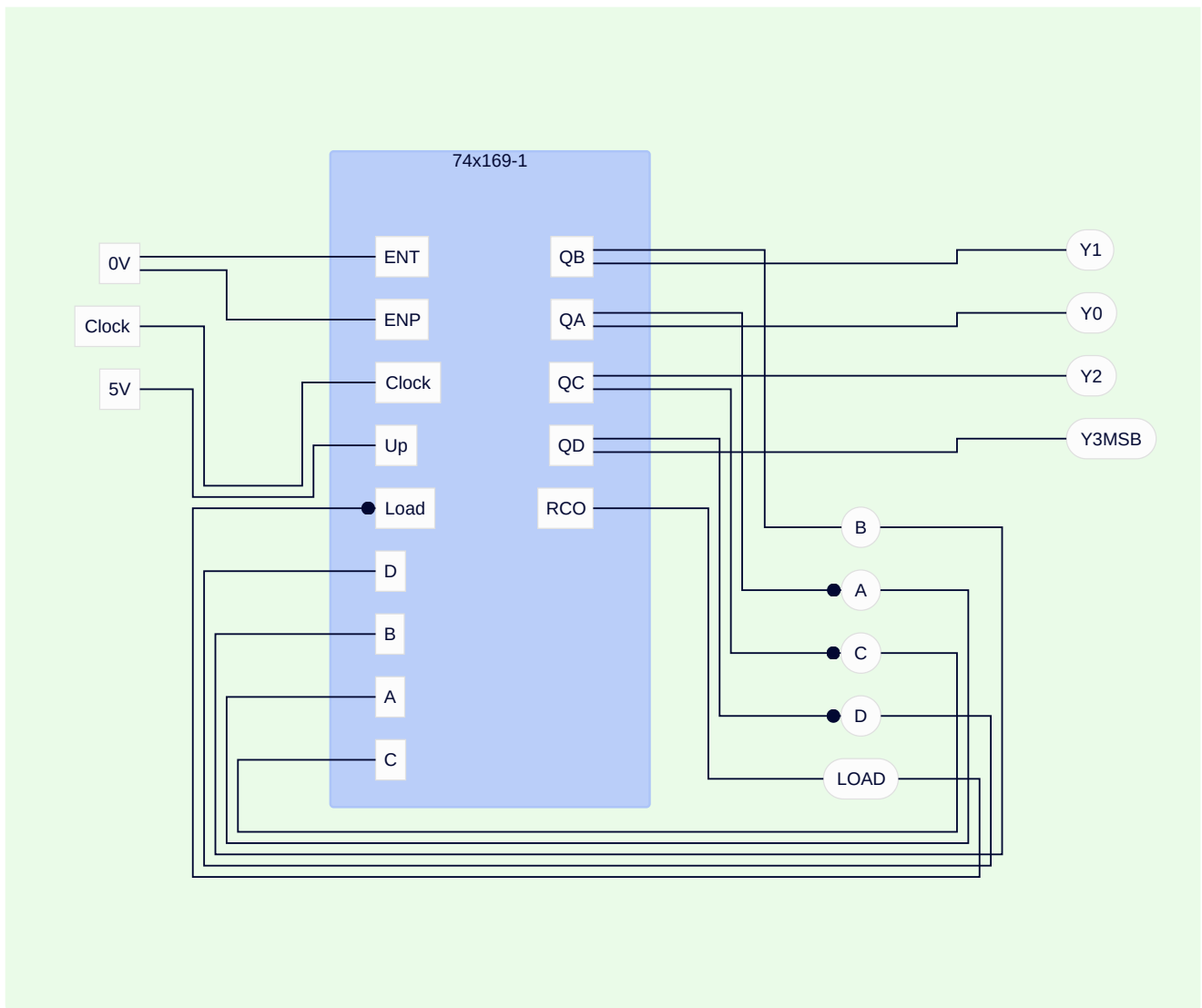

Code

tbird_fsm.sv

```
typedef enum logic [2:0] {
    IDLE = 3'b000,
    L1   = 3'b001,
    L2   = 3'b011,
    L3   = 3'b010,
    R1   = 3'b101,
    R2   = 3'b111,
    R3   = 3'b110,
    LR3  = 3'b100
} t_tbird_lights_state;

module tbird_fsm (
    input logic      clk,
    input logic      rst_b,
    input logic      left,
    input logic      right,
    input logic      haz,
```



```

output logic [2:0] l_lights,
output logic [2:0] r_lights
);
t_tbird_lights_state state;

always_ff @(posedge clk or negedge rst_b) begin
    if (~rst_b)
        state ≤ IDLE;
    else
        case (state)
            IDLE: begin
                if ( (left & right) | haz)
                    state ≤ LR3;
                else if (left)
                    state ≤ L1;
                else if (right)
                    state ≤ R1;
                else
                    state ≤ IDLE;
            end
            L1: state ≤ haz ? LR3 : L2;
            L2: state ≤ haz ? LR3 : L3;
            L3: state ≤ IDLE;
            R1: state ≤ haz ? LR3 : R2;
            R2: state ≤ haz ? LR3 : R3;
            R3: state ≤ IDLE;
            LR3: state ≤ IDLE;
        endcase
end

always_comb begin
    case (state)
        IDLE: begin
            l_lights = 3'b000;
            r_lights = 3'b000;
        end
        L1: begin
            l_lights = 3'b001;
            r_lights = 3'b000;
        end
        L2: begin
            l_lights = 3'b011;
            r_lights = 3'b000;
        end
        L3: begin
            l_lights = 3'b111;
            r_lights = 3'b000;
        end
        R1: begin
            l_lights = 3'b000;

```

```

        r_lights = 3'b001;
    end
    R2: begin
        l_lights = 3'b000;
        r_lights = 3'b011;
    end
    R3: begin
        l_lights = 3'b000;
        r_lights = 3'b111;
    end
    LR3: begin
        l_lights = 3'b111;
        r_lights = 3'b111;
    end
endcase
end

endmodule

```

testbench_hw8.sv

```

module testbench_hw8 ();

    logic clk, rst_b, left, right, haz;
    logic [2:0] l_lights, r_lights;

    tbird_fsm UUT (
        clk, rst_b, left, right, haz, l_lights, r_lights
    );

    initial begin
        clk    = 1'b0;
        rst_b  = 1'b1;
        left   = 1'b0;
        right  = 1'b0;
        haz    = 1'b0;

        forever #5 clk = ~clk;
    end

    initial begin
        #10;
        rst_b = 1'b0;
        #20;
        rst_b = 1'b1;
        #20;
        right = 1'b1;
        #40;
    end

```

```
        right = 1'b0;
        left  = 1'b1;
        #40;
        left  = 1'b0;
        right = 1'b1;
        #10;
        right = 1'b0;
        haz   = 1'b1;
        #10;
        haz   = 1'b0;
        #10;
        right = 1'b1;
        #20;
        right = 1'b0;
        haz   = 1'b1;
        #10;
        haz   = 1'b0;
        #10;
        left  = 1'b1;
        #10;
        left  = 1'b0;
        haz   = 1'b1;
        #10;
        haz   = 1'b0;
        #10;
        left  = 1'b1;
        #20;
        left  = 1'b0;
        haz   = 1'b1;
        #10;
        haz   = 1'b0;
        #10;
        $finish();
    end
endmodule
```

Deliverables

