

10

8.48

Use the power information given for the circuit to determine:

Load \mathbf{Z}_1 : $24kW@pf = 0.66$ leading

Load \mathbf{Z}_2 : $18kW@pf = 0.82$ lagging

a

\mathbf{Z}_1 and \mathbf{Z}_2

✓ Answer ✓

$$S = \frac{P_{av}}{pf} = 21.95 \text{ kW}$$

$$\phi_z = \cos^{-1}(0.82) = 34.92^\circ$$

$$\mathbf{S} = 27 \angle 34.92^\circ \text{ kW}$$

$$\mathbf{Z} = \frac{\mathbf{V}\mathbf{V}^*}{\mathbf{S}} = \frac{|\mathbf{V}|^2}{\mathbf{S}}$$

$$\mathbf{Z}_2 = 8.82 \angle 34.92^\circ \Omega = 7.232 + 5.048i \Omega$$

$$\mathbf{I}_2 = \frac{\mathbf{V}_2}{\mathbf{Z}_2} = 49.89 \angle -34.92^\circ \text{ A}$$

$$\mathbf{V}_1 = \mathbf{I}_2(\mathbf{Z}_2 + 1.2 + 0.4i) = 500.833 \angle -2.05^\circ \text{ V} = 500.5 - 17.9i \text{ V}$$

$$S = 36 \text{ kW}$$

$$\phi_z = -48.70^\circ$$

$$\mathbf{S} = 36 \angle -48.70^\circ$$

$$\mathbf{Z}_1 = 4.599 + 5.235i \Omega$$

b

The rms value of \mathbf{V}_s

✓ Answer

$$\mathbf{I}_1 = \frac{\mathbf{V}_1}{\mathbf{Z}_1} = 63.93 + 67.72i \text{ A}$$

$$\mathbf{V}_s = 0.6\mathbf{I}_1 + \mathbf{V}_1 = 538.87 + 22.73i \text{ V} = 539.35 \angle 2.42^\circ \text{ V}$$

8.51

For the circuit, choose the load impedance \mathbf{Z}_L so that the power dissipated in it is a maximum. How much power will that be?

✓ Answer

With Z_L as an open circuit,

All the resistors simplify to $Z_{eq} = 6 - 2j \Omega$

$$I = 0.9 + 0.3j A$$

The below current will be $\frac{(4-2j)I}{1+2j} = 0.6 - 1.8j$

This means the voltage across $V_L = 5.4 + 1.8j$

$$P_{max} = \frac{V_L^2}{8(6)} = 0.54 + 0.405j = 0.675 W$$

8.55

✓ Answer

With Z_L as open,

$$I_x = 0.001667 A$$

$$\text{This makes } V_L = 4000I_x = 6.67 V$$

$$6000I_x + 2000I_x + 4000jI_L - 3000(I_x + I_L) - 15 = 0$$

$$5000I_x + (4000j - 3000)I_L = 15$$

$$I_x = I_L j$$

$$I_x = \frac{15}{9000 + 3000j}$$

$$I_L = 0.0005 + 0.0015j$$

$$Z_{Th} = 1.3 - 4j k\Omega$$

$$P_{max} = 4.278 mW$$

9.2

Determine the resonant frequency of the circuit shown given that

$$R = 100 \Omega$$

$$L = 5 mH$$

$$C = 1 \mu F$$

✓ Answer

$$\begin{aligned} Z_{eq} &= \omega Li + \frac{1}{\frac{1}{R} + i\omega C} = \frac{R + \omega Li - \omega^2 LRC}{1 + i\omega RC} \\ &= \frac{R + \omega Li - \omega^2 LRC - \omega R^2 Ci + \omega^2 LRC + \omega^3 LR^2 C^2 i}{1 + (\omega RC)^2} \end{aligned}$$

$$\mathcal{I}(Z_{eq}) = 0$$

$$= \frac{\omega L - \omega R^2 C + \omega^3 LR^2 C^2}{1 + (\omega RC)^2}$$

$$= L - R^2 C + \omega^2 LR^2 C^2$$

$$\frac{R^2 C - L}{LR^2 C^2} = \omega^2$$

$$\sqrt{\frac{1}{LC} - \frac{1}{R^2C^2}} = \omega$$

$$= 10000 \text{ rad/s}$$

9.6

✓ **Answer**

By KVL and KCL,

$$H = - \frac{iCL_1R\omega^2}{CL_1L_2\omega^3 - iCL_1R\omega^2 - L_1\omega - L_2\omega + iR}$$