

☐ **PHYS115** ☐ **PHYS121** ☐ **PHYS123**
☐ **PHYS116** ☒ **PHYS122** ☐ **PHYS124**
Lab Cover Letter

Author (You) Trevor N Signature: Trevor N

I declare that this assignment is original and has not been submitted for assessment elsewhere, and acknowledge that the assessor of this assignment may, for the purpose of assessing this assignment: (1) reproduce this assignment and provide a copy to another member of faculty; and/or (2) communicate a copy of this assignment to a plagiarism checking service (which may then retain a copy of this assignment on its database for the purpose of future plagiarism checking).

Lab Partner(s) Lauren Lee, Koki Takizawa

Date Performed 2024-11-18 Date Submitted 12-21

Lab (such as #1: UNC) #6 LCR

TA: El

GRADE (to be filled in by your TA) See your TA for detailed feedback.
 An 'x' next to a subcategory means you need to improve this aspect of your work.

Paper Subtotals (points)

- | | |
|--|--|
| <p>() General (6)</p> <p>_____ Sig. figs.</p> <p>_____ Units</p> <p>_____ Clarity of Presentation</p> <p>_____ Format</p> <p>() Abstract (4)</p> <p>_____ Quantity or principle</p> <p>_____ How measurement was made</p> <p>_____ Numerical Results</p> <p>_____ Conclusion</p> <p>() Intro & Theory (9)</p> <p>_____ Basic principle</p> <p>_____ Main equations to be used</p> <p>_____ Apparatus</p> <p>_____ What will be plotted</p> <p>_____ Fitting parameters related</p> <p>() Exp. Procedures (15)</p> <p>_____ Description</p> <p>_____ Stating and justifying uncertainties</p> <p>_____ Data Record</p> <p>_____ Quality of Lab Work</p> <p>() Analysis & Error Analysis (20)</p> <p>_____ Discussion</p> <p>_____ Equations & Calculations</p> <p>_____ Presentation inc. Graphs, Tables</p> <p>_____ Results Reported & Reasonable</p> <p>_____ Underlined items addressed</p> | <p>() Discussion & Conclusions (6)</p> <p>_____ Numerical comparison of results</p> <p>_____ Logical conclusions</p> <p>_____ Discussion of pos. errors</p> <p>_____ Suggestions to reduce errors</p> <p>() Paper Total (60 points)
 (30 points for CME or EPF)</p> <p>() Notebook (10 points)</p> <p>_____ Format (<i>proper style, following directions</i>)</p> <p>_____ Apparatus (<i>brief description of equipment, including sketches</i>)</p> <p>_____ Data (<i>including computer file names and manually recorded data</i>)</p> <p>_____ Experimental Technique (<i>describing your procedures; stating & justifying uncersts.</i>)</p> <p>_____ Analysis (<i>results and errors</i>)</p> <p>() Worksheet(s)/Fill-in-the-Blank-Report (30 points) if applicable</p> <p>() Adjustments – late submissions, improper procedures, etc. – or bonus points for exceptional work.</p> <p>() Total Grade</p> <p>Graded by _____ (TA's initial)</p> |
|--|--|

PHYS 122-119B Lab 6: LCR

Trevor Nichols, Lauren Lee, Koki Takizawa
PHYS 122-119B
Station 32, Rockefeller 403
Lab 6: LCR (Damped and Forced Oscillator)
2024-11-18T10:36:50-04:00

Department of Physics,
Case Western Reserve University,
Cleveland, Ohio,
44106-7079

1 Abstract

The purpose of this lab is to observe and model the oscillatory nature of the LC circuit, by observing its natural resonance frequency, then testing if forcing other frequencies on the circuit diminishes its output if not at our expected resonance frequency.

Results:

	$C = C_1$ $R = R_C$	$C = C_2$ $R = R_C$	$C = C_2$ $R = R_C + R_1$	$C = C_2$ $R = R_C + R_2$
$\tau_{experimental}$	0.00080 ± 0.00002	0.0008 ± 0.00001	0.0006 ± 0.00001	0.000195 ± 0.00000
$\omega'_{experimental}$	-23280 ± 20	-4950 ± 10	-4730 ± 10	-5979 ± 6
$\tau_{expected}$	0.00092 ± 0.00002	0.00092 ± 0.00002	0.00061 ± 0.00001	0.000260 ± 0.00000
$\omega'_{expected}$	22900 ± 300	5110 ± 70	5260 ± 70	6310 ± 70

Variable	Value
$Q_{experimental}$	-3.05 ± 0.05
$\omega_{Rexperimental}$	-49.4 ± 0.1
$Q_{expected}$	3.67 ± 0.06
$\omega_{Rexpected}$	48.9 ± 0.7

We fail to reject the null hypothesis that our experimental data follows the current accepted theory.

2 Theory

2.1 Constants

L	Inductance of a coil
Q	Charge within a capacitor
R	Resistance of a resistor
C	Capacitance of a capacitor
ω_R	Resonant frequency of an LC circuit
τ	Decay rate of an LC circuit
V_C	Voltage across a capacitor
Q_u	Quality factor of a response curve

2.2 Formulae

2.2.1 Damped Oscillator

Given the expected behavior of an inductor, capacitor, and capacitor, we may find that the charge within the capacitor follows the oscillatory differential equation below, with the capacitor having an initial charge of Q_0 .

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0 \quad \text{Expected behavior of LC} \quad (2.2.1.1)$$

$$Q = Q_0 e^{-t/\tau} \sin(\omega' t + \phi) \quad \text{Gen. sol. of damped oscillator} \quad (2.2.1.2)$$

$$\tau = \frac{2L}{R} \quad \text{Decay rate} \quad (2.2.1.3)$$

$$\omega = \frac{1}{\sqrt{LC}} \quad \text{Freq. of undamped osci.} \quad (2.2.1.4)$$

$$\omega' = \sqrt{\omega^2 - \frac{1}{\tau^2}} \quad \text{Freq. of damped osci.} \quad (2.2.1.5)$$

$$Q = CV_C \quad \text{Charge in a capacitor} \quad (2.2.1.6)$$

$$V_C = \frac{Q_0}{C} e^{-t/\tau} \sin(\omega' t + \phi) \quad \text{Gen. sol. of damped oscillator} \quad (2.2.1.7)$$

2.2.2 Forced Oscillator

Now, instead of just "releasing" the circuit after charging the capacitor, we instead force the circuit with a constant sine curve of amplitude V_m , and thus our differential equation will be updated to reflect that.

$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = V_m \sin(\omega t)$	Behavior of forced LC	(2.2.2.1)
$Q = \frac{V_m}{\sqrt{\left(\frac{1}{C} - L\omega^2\right)^2 + R^2\omega^2}} \sin(\omega t + \phi)$	General solution	(2.2.2.2)
$\max_{\omega} Q = \frac{V_m}{R\omega} \sin(\omega t + \phi)$	Maximize Q	(2.2.2.3)
$\max_{\omega} Q \implies \frac{1}{C} = L\omega^2$	Corresponding omega	(2.2.2.4)
$\omega = \frac{1}{\sqrt{LC}} = \omega_R$	Max Q implies resonance	(2.2.2.5)
$I = \frac{dQ}{dt}$	Definition of current	(2.2.2.6)
$I = \frac{V_m}{\sqrt{\left(\frac{1}{\omega C} - L\omega\right)^2 + R^2}} \sin(\omega t + \phi')$	General solution	(2.2.2.7)
$\frac{V_R}{V_m} = \frac{R}{\sqrt{\left(\frac{1}{\omega C} - L\omega\right)^2 + R^2}}$	Solve for gain	(2.2.2.8)

Now, given the width $\Delta\omega$ at half the maximum of the curve, we may determine Q_u , the quality

$Q_u = \frac{\omega_R L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$	Definition of quality	(2.2.2.9)
$\frac{V_R}{V_m} = \frac{R}{\sqrt{\left(\frac{L}{\omega}(\omega_R^2 - \omega^2)\right)^2 + R^2}}$	In terms of resonant freq.	(2.2.2.10)
$\frac{V_R}{V_m} = \frac{\frac{R}{L}}{\sqrt{(\omega_R^2 - \omega^2)^2 + \frac{\omega_R^2 \omega^2}{Q_u^2}}}$	In terms of Q	(2.2.2.11)
$\frac{V_R}{V_m} = \frac{\frac{RQ_u}{L\omega_R\omega}}{\sqrt{\left(Q_u \frac{\omega_R^2 - \omega^2}{\omega_R\omega}\right)^2 + 1}}$	Simplify gain	(2.2.2.12)
$\frac{V_R}{V_m} = \frac{A}{\sqrt{\left(Q_u \frac{\omega_R^2 - \omega^2}{\omega_R\omega}\right)^2 + 1}}$	$A \approx 1$ around resonance	(2.2.2.13)
$\frac{1}{2} = \frac{\frac{R}{L}}{\sqrt{(\omega_R^2 - \omega^2)^2 + \frac{\omega_R^2 \omega^2}{Q_u^2}}}$	Set half gain from 2.2.2.11	(2.2.2.14)
$(\omega_R^2 - \omega^2)^2 + \frac{\omega_R^2 \omega^2}{Q_u^2} = 4 \frac{\omega_R^2 \omega^2}{Q_u^2}$	Using max I	(2.2.2.15)
$(\omega_R^2 - \omega^2)^2 = 3 \frac{\omega_R^2 \omega^2}{Q_u^2}$	Solving for Qu	(2.2.2.16)
$\omega_R^2 - \omega^2 = \sqrt{3} \frac{\omega_R \omega}{Q_u}$		(2.2.2.17)
$\frac{1}{2} \Delta\omega = \frac{\sqrt{3}}{2} \frac{\omega_R}{Q_u}$	Approximate omega	(2.2.2.18)
$\frac{\Delta\omega}{\omega_R} = \frac{\sqrt{3}}{Q_u}$	Solve for Qu	(2.2.2.19)
$\Delta\omega = \frac{\sqrt{3}R}{L}$	From 2.2.2.9	(2.2.2.20)

2.3 Error Propagation

2.3.1 Damped Oscillator

$$V_C = \frac{Q_0}{C} e^{-t/\tau} \sin(\omega' t + \phi) \quad \text{From 2.2.1.7} \quad (2.3.1.1)$$

$$\tau = \frac{2L}{R} \quad \text{From 2.2.1.3} \quad (2.3.1.2)$$

$$\delta_\tau = \tau \sqrt{\left(\frac{\delta_L}{L}\right)^2 + \left(\frac{\delta_R}{R}\right)^2} \quad \text{Error prop.} \quad (2.3.1.3)$$

$$\omega = \frac{1}{\sqrt{LC}} \quad \text{From 2.2.1.4} \quad (2.3.1.4)$$

$$\omega' = \sqrt{\omega^2 - \frac{1}{\tau^2}} \quad \text{From 2.2.1.5} \quad (2.3.1.5)$$

$$\omega' = \sqrt{\frac{1}{LC} - \frac{1}{\tau^2}} \quad \text{Substitute} \quad (2.3.1.6)$$

$$\delta_{\omega'} = \frac{1}{2\omega'} \sqrt{\left(\frac{\delta_L}{L^2 C}\right)^2 + \left(\frac{\delta_C}{LC^2}\right)^2 + \left(\frac{2\delta_\tau}{\tau^3}\right)^2} \quad \text{Substitute} \quad (2.3.1.7)$$

2.3.2 Forced Oscillator

$$\frac{V_R}{V_m} = \frac{A}{\sqrt{\left(Q \frac{\omega_R^2 - \omega^2}{\omega_R \omega}\right)^2 + 1}} \quad \text{From 2.2.2.13} \quad (2.3.2.1)$$

$$Q_u = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \text{From 2.2.2.9} \quad (2.3.2.2)$$

$$\delta_{Q_u} = Q_u \sqrt{\left(\frac{\delta_R}{R}\right)^2 + \left(\frac{\delta_L}{2L}\right)^2 + \left(\frac{\delta_C}{2C}\right)^2} \quad \text{Error Prop.} \quad (2.3.2.3)$$

$$\omega_R = \frac{1}{\sqrt{LC}} \quad \text{From 2.2.2.5} \quad (2.3.2.4)$$

$$\delta_{\omega_R} = \omega_R \sqrt{\left(\frac{\delta_L}{2L}\right)^2 + \left(\frac{\delta_C}{2C}\right)^2} \quad \text{Error Prop.} \quad (2.3.2.5)$$

3 Procedure

3.1 Materials

1. 80 – 100 mH inductor
2. 2x 1 $k\Omega$ resistors
3. 100 Ω resistor
4. 0.47 μF capacitor
5. 0.022 μF capacitor
6. DMM
7. Oscilloscope
8. Function generator

3.2 General Setup


3.2.1 Damped Oscillator

For each of the following RC combinations:

1. $C = 0.022 \mu F, R = 0 \Omega$
2. $C = 0.47 \mu F, R = 0 \Omega$
3. $C = 0.47 \mu F, R = 100 \Omega$
4. $C = 0.47 \mu F, R = 500 \Omega$

We performed the following:

1. Set up this diagram:

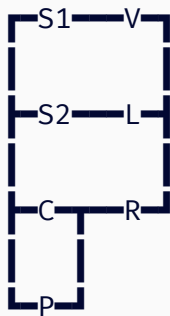


- I. $S1, S2$ are switches (open by default)
 - II. V is our battery
 - III. L is our induction coil
 - IV. C is our capacitor
 - V. R is our added resistance
 - VI. P is our voltage probe
2. Charge the capacitor by activating $S1$
 3. Begin collecting data with P
 4. Deactivate $S1$ and activate $S2$ to allow the LCR circuit to enter damped oscillation
 5. Fit the voltage vs. time data to eq. 2.2.1.7
 6. Check if our ω' and τ matches expectations
 7. Classify if this system is over, under, or critically damped by the value of ω'

3.2.2 Forced Oscillator

We performed the following:

1. Set up this diagram:

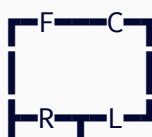



- I. F is our function generator set to a sine wave with frequency $f = \frac{\omega}{2\pi}$ and amplitude V_m
 - II. L is our induction coil
 - III. C is our capacitor
 - IV. R is our added resistance
 - V. P is our voltage probe
2. Activate the function generator at various frequencies
 3. Record the output amplitude of the sinusoidal on the probe
 4. Fit our frequency vs. amplitude data with eq. 2.2.2.13
 5. Check if our fit values match the expected results

4 Analysis

4.1 Damped Oscillator

With the following constants:

$$R_1 = 98.9 \pm 0.5\% \Omega$$

$$R_2 = 0.49 \pm 0.5\% k\Omega$$





$$R_C = 193.6 \pm 0.5\% \Omega$$

$$L = 88.8 \pm 2\% mH$$

$$C_1 = 21.6 \pm 2\% nF$$

$$C_2 = 0.451 \pm 2\% \mu F$$

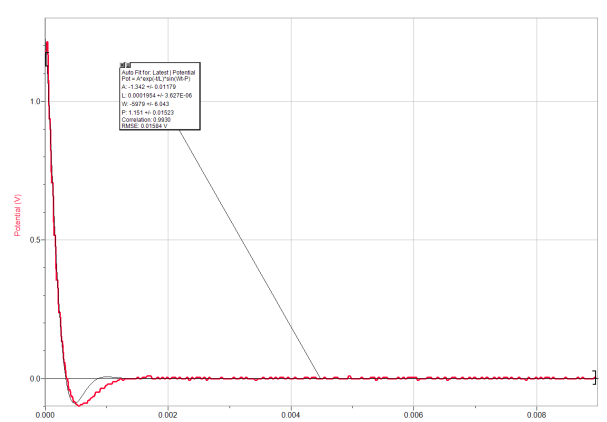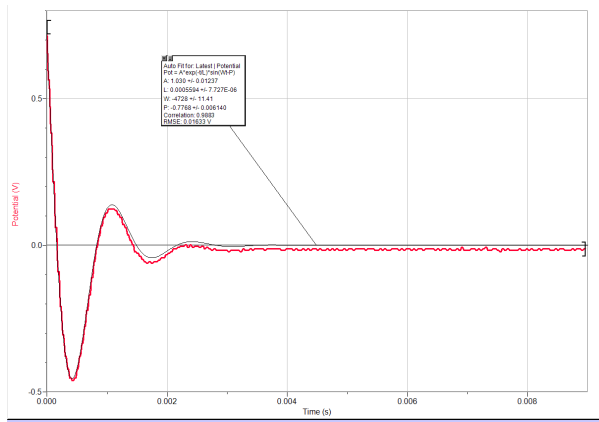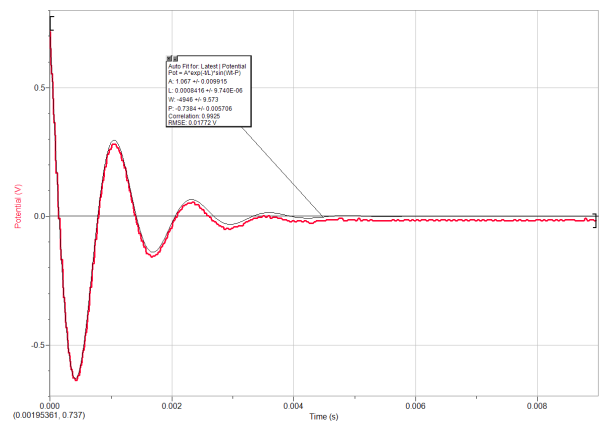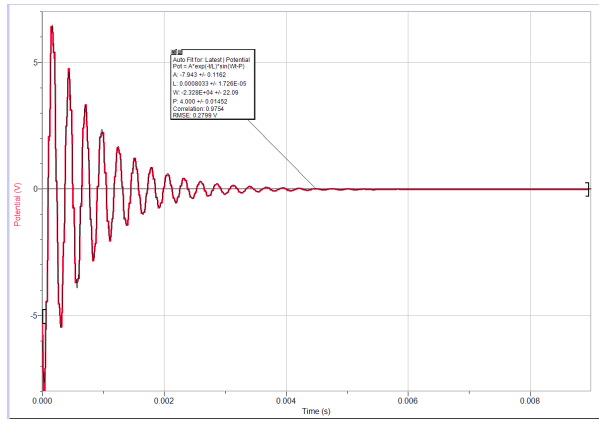With four trials with the following RC combinations, we fit our voltage vs. time data to eq. 2.2.1.7 and obtained the following fit values



	$C = C_1$ $R = R_C$	$C = C_2$ $R = R_C$	$C = C_2$ $R = R_C + R_1$	$C = C_2$ $R = R_C + R_2$
$\frac{Q_0}{C}$ (V)	-7.9 ± 0.1	1.07 ± 0.01	1.03 ± 0.01	-1.34 ± 0.01
τ	0.00080 ± 0.00002	0.0008 ± 0.00001	0.0006 ± 0.00001	0.000195 ± 0.000004
ω'	-23280 ± 20	-4950 ± 10	-4730 ± 10	-5979 ± 6
ϕ	4.00 ± 0.01	-0.738 ± 0.006	-0.777 ± 0.006	1.15 ± 0.02

Using eq. 2.3.1.2, 2.3.1.3, 2.3.1.6, and 2.3.1.7, we obtain our expected results of:

	$C = C_1$ $R = R_C$	$C = C_2$ $R = R_C$	$C = C_2$ $R = R_C + R_1$	$C = C_2$ $R = R_C + R_2$
τ	0.00092 ± 0.00002	0.00092 ± 0.00002	0.00061 ± 0.00001	0.000260 ± 0.000005
ω'	22900 ± 300	5110 ± 70	5260 ± 70	6310 ± 70

We find all our calculated values to be within around 3 to 6 standard deviations away from our experimental values, which is relatively close, and thus fail to reject the null hypothesis that our data matches the current expected values. Since all of our ω'^2 values are positive, all of these are underdamped.

4.2 Forced Oscillator

With the following constants:

$$R = 0.99 \pm 0.5\% \text{ k}\Omega$$


$$R_C = 193.6 \pm 0.5\% \Omega$$

$$L = 88.8 \pm 2\% \text{ mH}$$

$$C = 0.0047 \pm 2\% \mu\text{F}$$

$$V_{in} = 16.000 \text{ V}$$

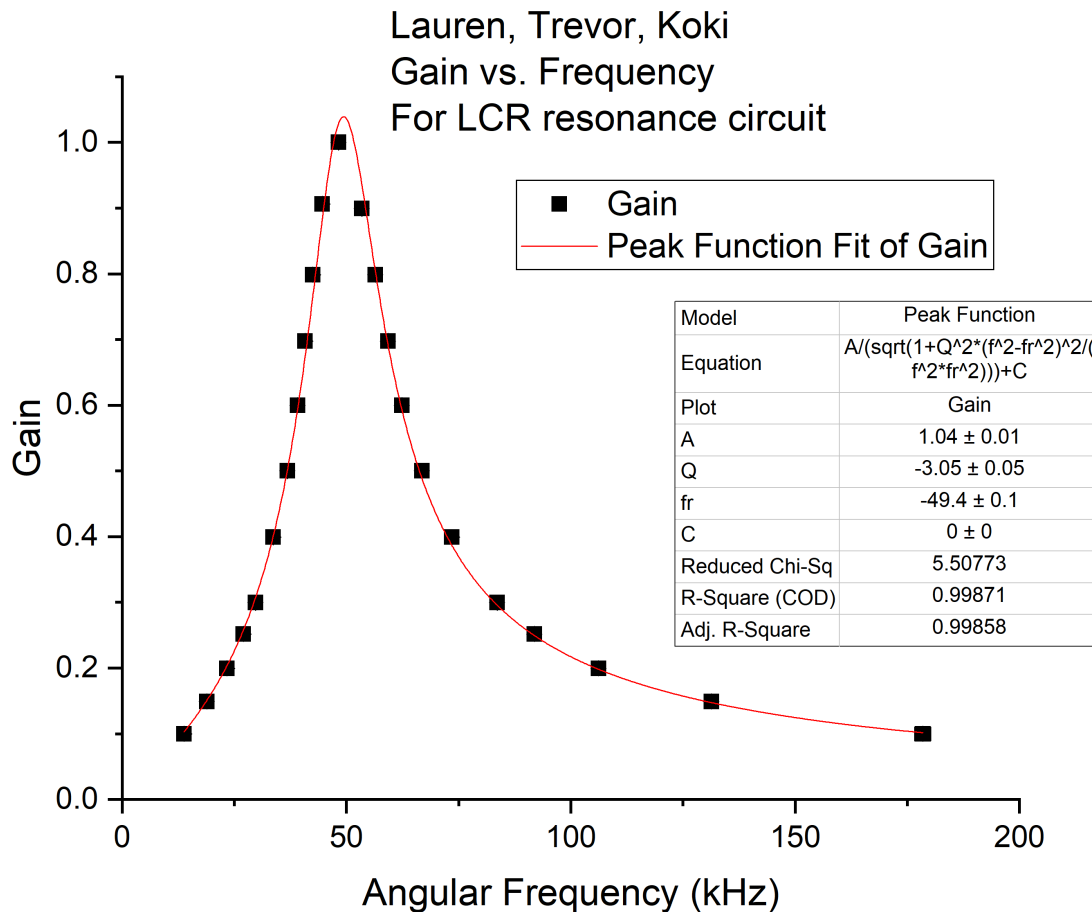After measuring the output amplitude at various frequencies, we obtain the following graph of gain $\frac{V_R}{V_m}$ vs. angular frequency ω .



This gives us the fit values fit to the equation of 2.2.2.13:

Variable	Value
Q_u	-3.05 ± 0.05
ω_R	-49.4 ± 0.1

Using the eq. 2.3.2.2, 2.3.2.3, 2.3.2.4, and 2.3.2.5 we are able to calculate the expected values for Q_u and ω_R

Variable	Value
Q_u	3.67 ± 0.06
ω_R	48.9 ± 0.7

We find that our experimental values align fairly closely to our expected values, with our Q_u value being within 10 SD of our experimental value, and our ω_R being within 1 SD of our experimental value. Thus, we fail to reject the null hypothesis that our experiment follows the relevant theory.

5 Conclusion

In the purpose to observe and model the oscillatory nature of the LCR circuit, we fail to disprove the current theory of LCR circuits.

For the Damped Oscillator setup, we obtained the following values:

	$C = C_1$ $R = R_C$	$C = C_2$ $R = R_C$	$C = C_2$ $R = R_C + R_1$	$C = C_2$ $R = R_C + R_2$
$\tau_{experimental}$	0.00080 ± 0.00002	0.0008 ± 0.00001	0.0006 ± 0.00001	0.000195 ± 0.00000
$\omega'_{experimental}$	-23280 ± 20	-4950 ± 10	-4730 ± 10	-5979 ± 6
$\tau_{expected}$	0.00092 ± 0.00002	0.00092 ± 0.00002	0.00061 ± 0.00001	0.000260 ± 0.00000
$\omega'_{expected}$	22900 ± 300	5110 ± 70	5260 ± 70	6310 ± 70

For the Forced Oscillator setup, we obtained the following values:

Variable	Value
$Q_{uexperimental}$	-3.05 ± 0.05
$\omega_{Rexperimental}$	-49.4 ± 0.1
$Q_{uexpected}$	3.67 ± 0.06
$\omega_{Rexpected}$	48.9 ± 0.7

We find that all of our values are very close to the expected values, to within around 6 SD of the value. Thus, we fail to reject the null hypothesis that our experimental values follow the expected relations. We could possibly reduce error by being more careful to tare our tools before beginning the experiment, as well as taking significantly more data points, instead of merely 5 total. Overall, we find our data to be very close to what is expected.

6 Acknowledgements and Info

- Lab 6 - LCR
- 2024-11-18
- Station 32 Rockefeller 403
- PHYS 122-119B

Lab Partner: Lauren Lee, Koki Takizawa

Lab Manual: Lab 6 LCR PHYS 122

6.1 References

Driscoll, D., *General Physics 2: Electricity and Magnetism Lab Manual*, "Electric Potential and Fields".

Lab 6: LCR

$$R_1 = 98.9 \pm 0.5\% \Omega$$

$$R_2 = 0.49 \pm 0.5\% \text{ k}\Omega$$

$$R_c = 193.6 \pm 0.5\% \Omega$$


$$L = 88.8 \pm 2\% \text{ mH}$$

$$C_1 = 21.5 \text{ nF} \pm 2\%$$

$$C_2 = 0.451 \mu\text{F} \pm 2\%$$

This lab is about running the oscillation & decay for LCR circuits.

Procedure:

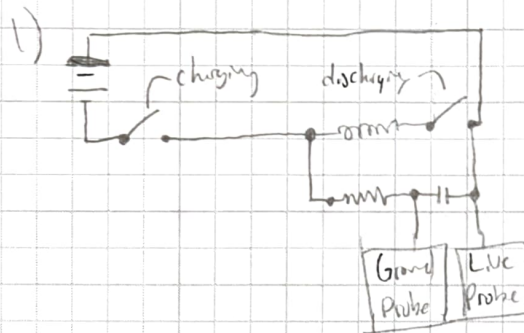

2) Swap out the capacitor & resistor to various values

3) Charge, then measure the discharge over time

4) Fit the result to $y = A e^{-t/\tau} \sin(\omega t - \phi)$

5) Calculate $\omega = 1/\sqrt{LC}$ and $\omega' = \sqrt{\omega^2 - 1/\tau^2}$ for both fitted & calculated values

6) Compare ω' & τ for both data.

$C = 21.5 \text{ nF} \pm 2\%$	$C = 0.451 \mu\text{F} \pm 2\%$	$C = 0.451 \mu\text{F} \pm 2\%$	$C = 0.451 \mu\text{F} \pm 2\%$
$R = 98.9 \pm 0.5\%$	$R = 98.9 \pm 0.5\%$	$R = 98.9 \pm 0.5\%$	$R = 98.9 \pm 0.5\%$

(τ)

(ω)

	$C = 21.5 \text{ nF} \pm 2\%$	$C = 0.451 \mu\text{F} \pm 2\%$	$C = 0.451 \mu\text{F} \pm 2\%$	$C = 0.451 \mu\text{F} \pm 2\%$
A	7.943 ± 0.1162	1.067 ± 0.009915	1.030 ± 0.01227	1.342 ± 0.01179
L	0.0008033 ± 0.0001726	0.0008416 ± 0.0000974	0.0005544 ± 0.00007727	0.0001954 ± 0.00003627
W	2328 ± 22.09	4946 ± 9.573	4728 ± 11.41	5979 ± 6.048
P	4.000 ± 0.01452	-0.7884 ± 0.005706	-0.7768 ± 0.006148	1.151 ± 0.01523

$$\delta\omega' = \sqrt{\left(\frac{\omega}{\omega'}\right)^2 + \left(\frac{1/\tau^2}{\omega'^2}\right)^2}$$

$$= \frac{1}{\omega'} \sqrt{\left(\frac{\omega}{\omega'}\right)^2 + \left(\frac{1/\tau^2}{\omega'^2}\right)^2}$$

$$\delta\omega = \frac{1}{2\omega} \left[\left(\frac{1}{L^2}\right)^2 + \left(\frac{1}{C^2}\right)^2 \right]^{1/2}$$


$$\delta\tau = \tau \left[\left(\frac{1}{L^2}\right)^2 + \left(\frac{1}{R^2}\right)^2 \right]^{1/2}$$

$$R = 0.99 \pm 0.5\% \text{ k}\Omega$$

$$L = 88.8 \pm 2\% \text{ mH}$$

$$C = \cancel{0.0047} \mu\text{F}$$

$$0.0047 \pm 2\% \mu\text{F}$$

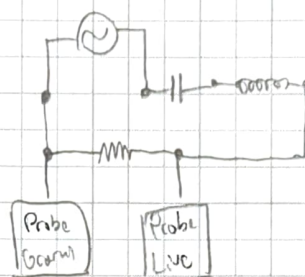

$$V_{in} = 16.000 \text{ V}$$

$$\text{Max Freq} = 7.67 \text{ kHz}$$

kHz Freq in	V V _{pp} out
7.67	11.12
2.20	1.11
28.4	1.11
10.63	5.56
5.86	5.56
3.72	2.22
16.9	2.22
13.3	3.33
4.73	3.33
5.36	4.44
11.7	4.44
9.92	6.67
6.22	6.67
6.493	7.76
9.43	7.76
8.98	8.88
6.77	8.88
7.1	10.08
8.5	10.00
3.0	1.66
20.9	1.66
14.62	2.80
4.3	2.80

- 1) Assemble circuit
- 2) Vary Function generator frequency
- 3) Find max out put w/ Probe
(at its corresponding freq)
- 4) Record frequency for out put voltages of
10%, 15, 20, 25, 30, 40, 50, 60, 70, 80, 90% of
max voltage
- 5) Plot freq vs. output V, fit this curve.
- 6) Fit data