

11

9.17

Generate Bode magnitude and phase plots (straight-line approximations) for the following voltage transfer functions


a

$$\mathbf{H}(\omega) = \frac{30(10+j\omega)}{(200+j2\omega)(1000+j2\omega)}$$

✓ Answer ✓

$$\begin{aligned}\mathbf{H}(\omega) &= \frac{30(10+j\omega)}{(200+j2\omega)(1000+j2\omega)} \\ &= \frac{\frac{3}{2000}(1+\frac{1}{10}j\omega)}{(1+\frac{1}{100}j\omega)(1+\frac{1}{500}j\omega)}\end{aligned}$$


ω	$\log \omega$	M	$\frac{dM}{d\omega} + \frac{dB}{decade}$
0	$-\infty$	$20 \log \left(\frac{3}{2000} \right)$	0
10	1	$20 \log \left(\frac{3}{2000} \right)$	20
100	2	$20(\log \left(\frac{3}{2000} \right) + 1)$	0
500	2.6990	$20(\log \left(\frac{3}{2000} \right) + 1)$	-20

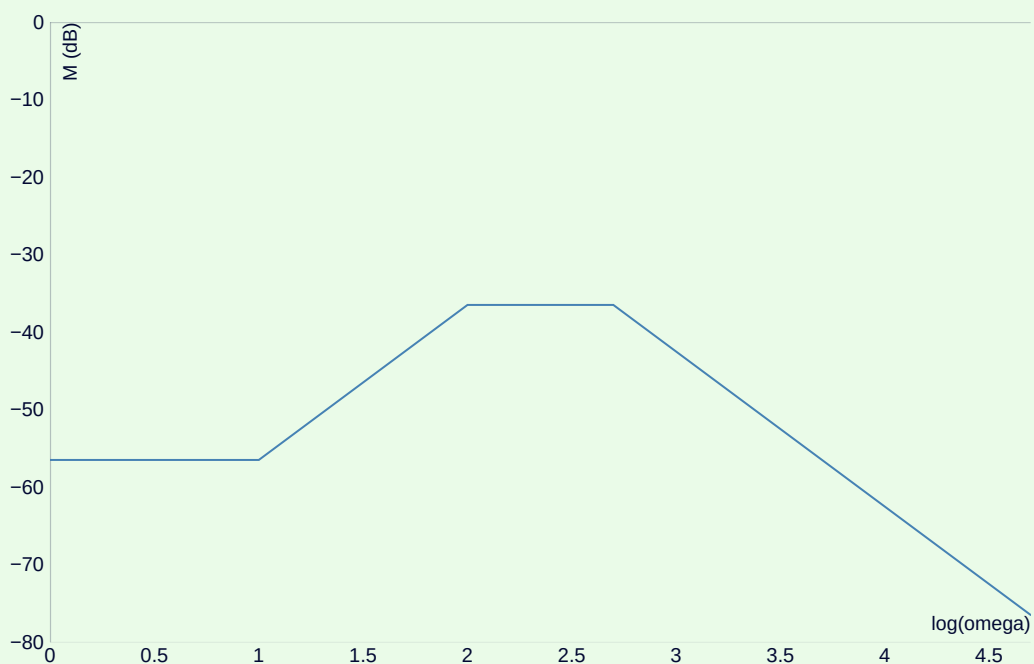

Component	$0.1\omega_c$	$10\omega_c$
$1 + \frac{1}{10}j\omega$	1	100

Component	$0.1\omega_c$	$10\omega_c$
$(1 + \frac{1}{100}j\omega)^{-1}$	10	1000
$(1 + \frac{1}{500}j\omega)^{-1}$	50	5000

ω	$\log \omega$	ϕ°	$\frac{d\phi}{d\omega} + \frac{^\circ}{decade}$
0	$-\infty$	0	0
1	0	0	45
10	1	45	0
50	1.6990	45	-45
100	2	$45(1 - \log 2)$	-90
1000	3	$45(-1 - \log 2)$	-45
5000	4.6990	-90	0

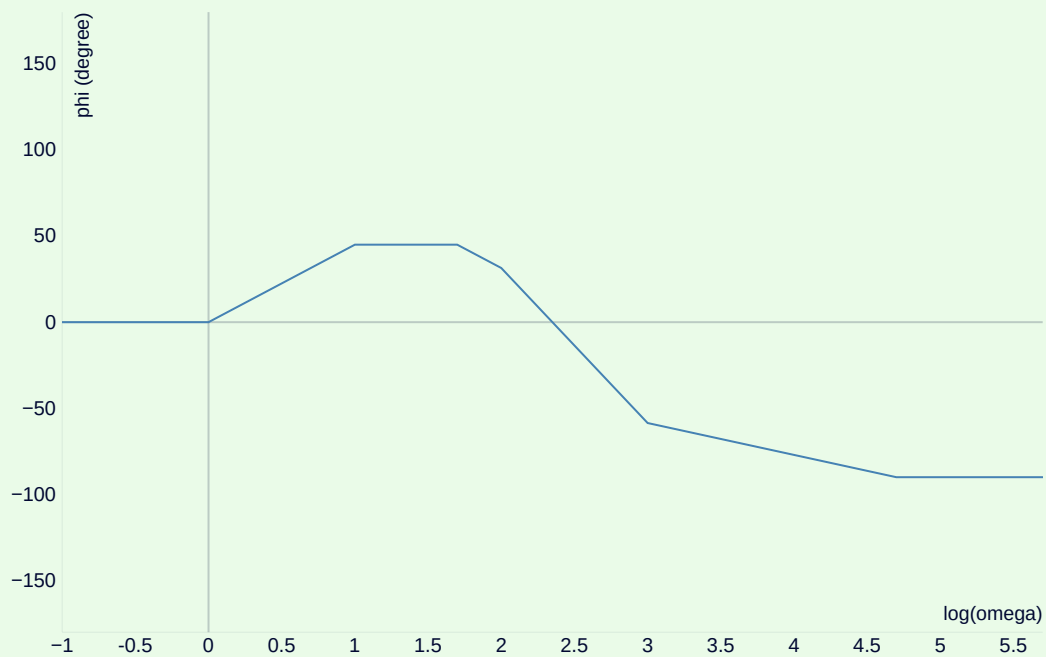


b

$$\mathbf{H}(\omega) = \frac{j100\omega}{(100+j5\omega)(100+j\omega)^2}$$

✓ Answer


$$\begin{aligned}\mathbf{H}(\omega) &= \frac{j100\omega}{(100+j5\omega)(100+j\omega)^2} \\ &= \frac{1}{10000} \frac{j\omega}{(1+\frac{1}{20}j\omega)(1+\frac{1}{100}j\omega)^2}\end{aligned}$$

ω	$\log \omega$	M	$\frac{dM}{d\omega} + \frac{dB}{decade}$
1	0	$20(-4)$	20
20	1.3010	$20(\log(2) - 3)$	0
100	2	$20(\log(2) - 3)$	-40

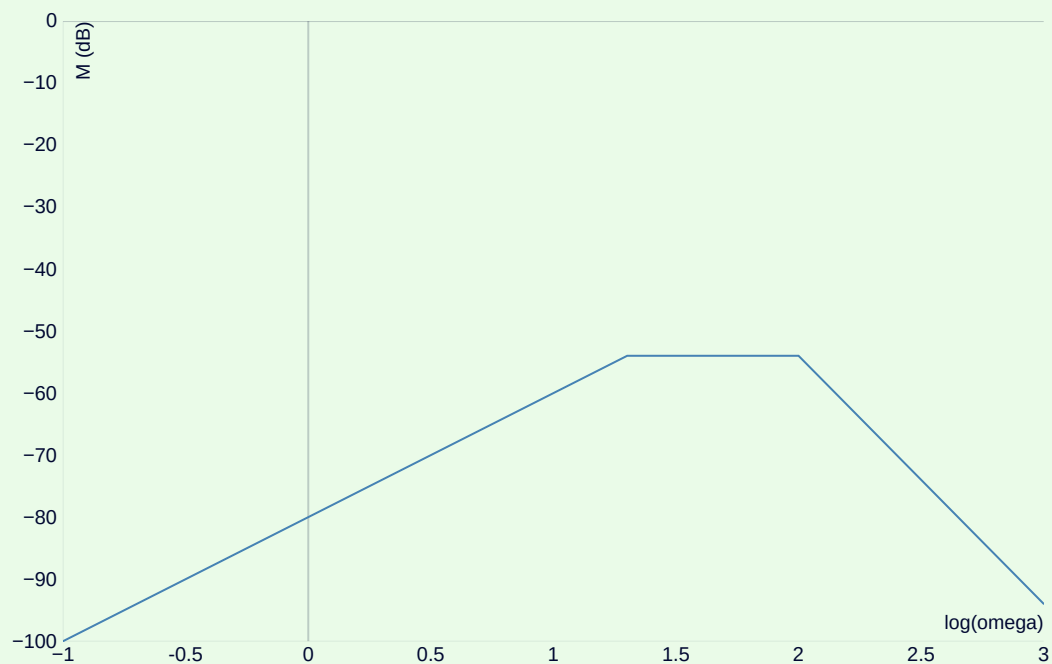

Component	$0.1\omega_c$	$10\omega_c$
$(1 + \frac{1}{20}j\omega)^{-1}$	2	200
$(1 + \frac{1}{100}j\omega)^{-1}$	10	1000

ω	$\log \omega$	ϕ°	$\frac{d\phi}{d\omega} + \frac{^\circ}{decade}$
0	$-\infty$	90	0
2	0.3010	90	-45
10	1	$90 - 45 \log(5)$	-90
200	2.3010	$90 - 45 \log(2000)$	-45
1000	3	-90	0

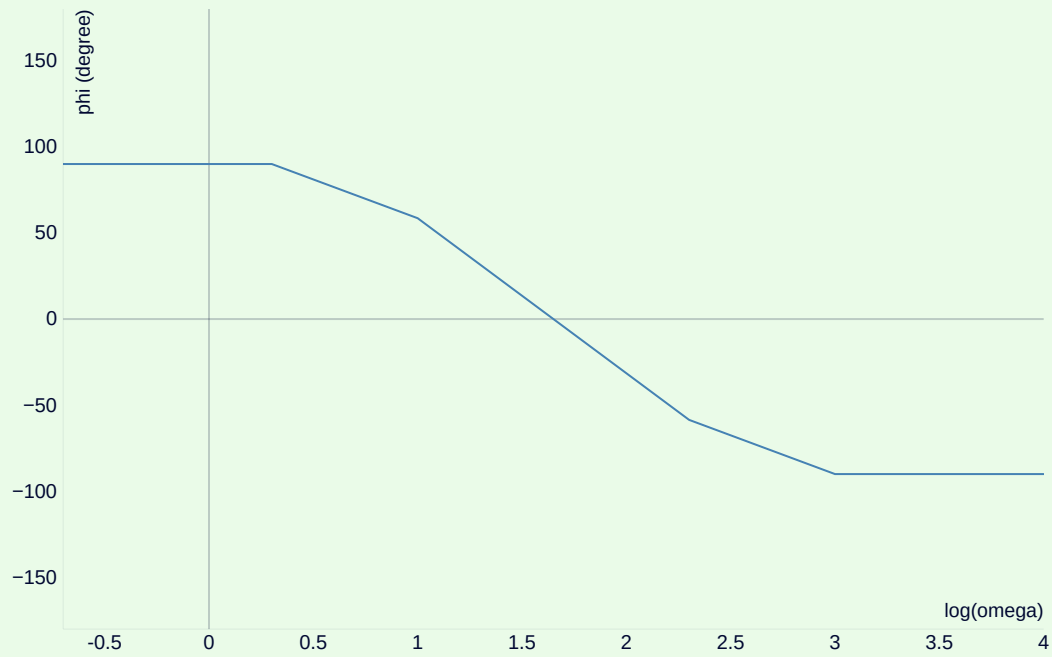


C

$$\mathbf{H}(\omega) = \frac{(200+j2\omega)}{(50+j5\omega)(1000+j\omega)}$$

✓ **Answer**


$$\begin{aligned} \mathbf{H}(\omega) &= \frac{(200+j2\omega)}{(50+j5\omega)(1000+j\omega)} \\ &= \frac{1}{250} \frac{1+\frac{1}{100}j\omega}{(1+\frac{1}{10}j\omega)(1+\frac{1}{1000}j\omega)} \end{aligned}$$

ω	$\log \omega$	M	$\frac{dM}{d\omega} + \frac{dB}{decade}$
0	$-\infty$	$20 \left(\log \left(\frac{1}{250} \right) \right)$	0
10	1	$20 \left(\log \left(\frac{1}{250} \right) \right)$	-20
100	2	$20 \left(\log \left(\frac{1}{250} \right) - 1 \right)$	0
1000	3	$20 \left(\log \left(\frac{1}{250} \right) - 1 \right)$	-20

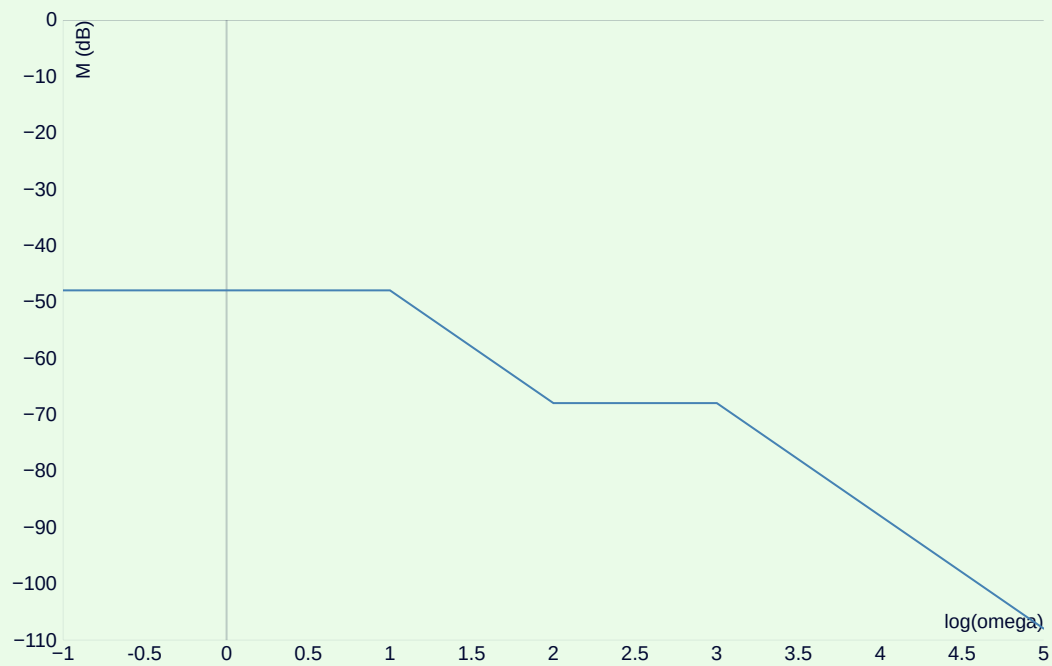

Component	$0.1\omega_c$	$10\omega_c$
$(1 + \frac{1}{10}j\omega)^{-1}$	1	100
$1 + \frac{1}{100}j\omega$	10	1000
$(1 + \frac{1}{1000}j\omega)^{-1}$	100	10000

ω	$\log \omega$	ϕ°	$\frac{d\phi}{d\omega} + \frac{^\circ}{decade}$
0	$-\infty$	0	0
1	0	0	-45
10	1	-45	0
100	2	-45	0
1000	3	-45	-45
10000	4	-90	0

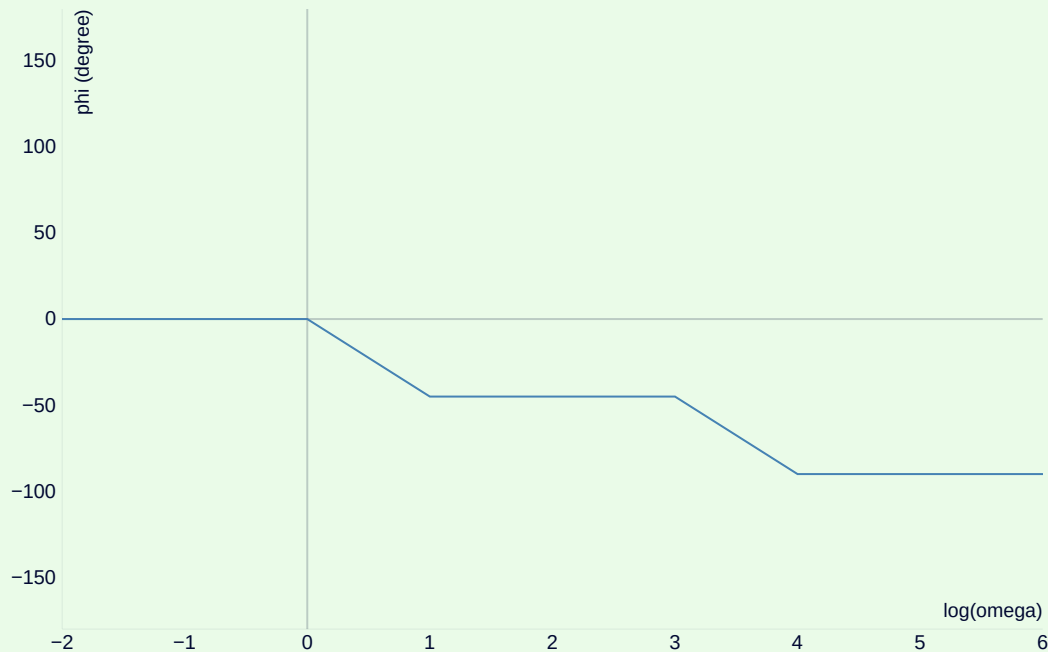

9.23

Determine the voltage transfer function $\mathbf{H}(\omega)$ corresponding to the Bode magnitude plot shown in **Fig. P9.23**. The phase of $\mathbf{H}(\omega)$ is 180° at $\omega = 0$.

✓ **Answer**

$$\mathbf{H}(\omega) = -20 \frac{(1 + \frac{1}{10}j\omega)(1 + \frac{1}{100}j\omega)}{j\omega}$$

9.35

For the circuit shown below

a

Obtain an expression for $\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i}$ in standard form

✓ **Answer**

$$\begin{bmatrix} iL\omega + R & -iL\omega \\ -iL\omega & iL\omega + R \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_i \\ 0 \end{bmatrix}$$

$$v_o = i_2 R$$

$$\mathbf{H}(\omega) = \frac{L\omega}{2L\omega - iR} = \frac{L}{R} \frac{i\omega}{1 + \frac{2L}{R}i\omega}$$


b

Generate spectral plots for the magnitude and phase of $\mathbf{H}(\omega)$, given that $R = 50\Omega$ and $L = 2\text{ mH}$.


✓ Answer

$$M(\omega) = \frac{L}{R} \frac{\omega}{\sqrt{1 + \frac{4L^2}{R^2}\omega^2}}$$
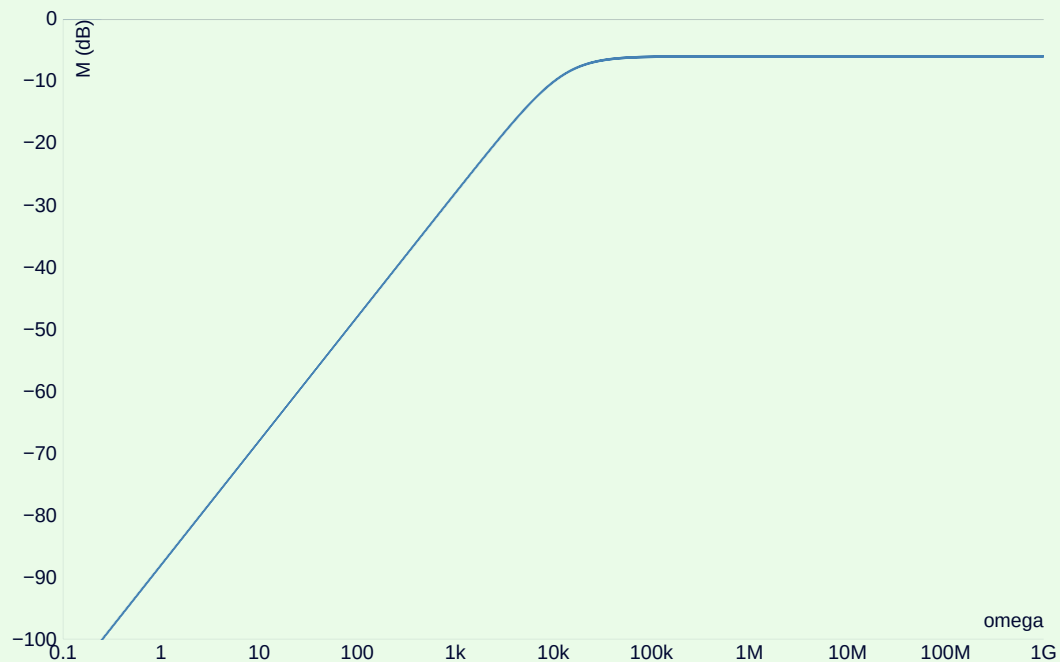
$$M(\omega)[dB] = 20 \log\left(\frac{L\omega}{R}\right) - 10 \log\left(1 + \frac{4L^2}{R^2}\omega^2\right)$$



$$\phi(\omega) = -\arctan(R, 2L\omega)$$

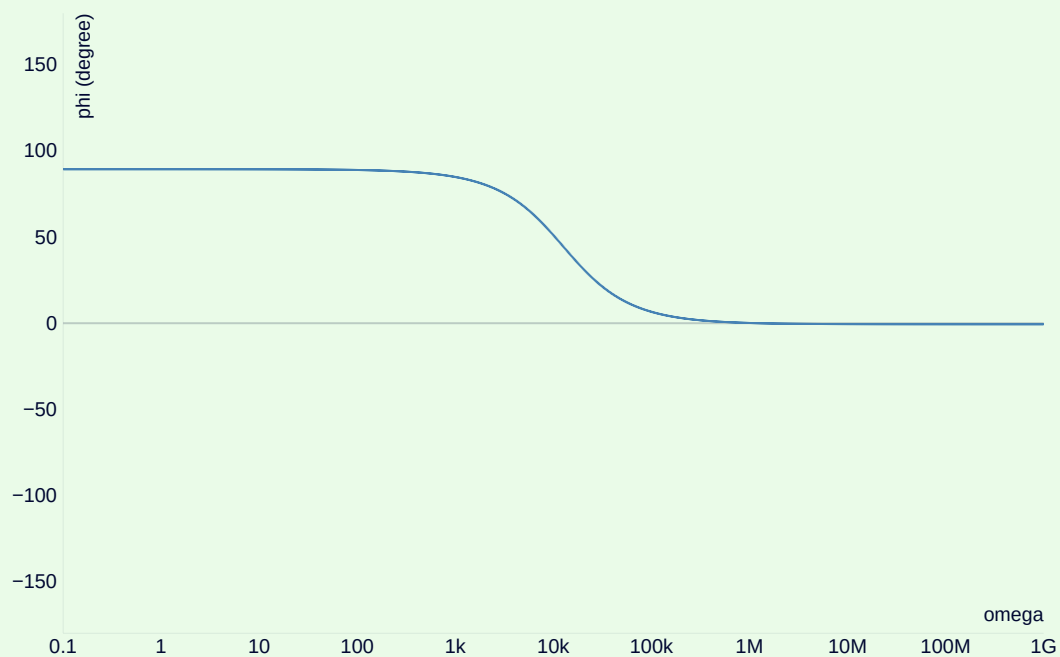

Determine the cutoff frequency ω_c and the slope of the magnitude (in dB) when $\frac{\omega}{\omega_c} \ll 1$

✓ **Answer**

$$\omega_c = \frac{2L}{R}$$

$$20 \frac{dB}{decade}$$

9.27

A series RLC circuit is drive by an ac source with a phasor voltage $\mathbf{V}_s = 10\angle 30^\circ V$. If the circuit resonates at 10^3 rad/s and the average power absorbed by the resistor at resonsnace is $2.5W$, determine the values of R, L, and C, given that $Q = 5$

✓ **Answer**

$$2.5 = \frac{10^2}{2R} \implies R = 20$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = 5$$

$$L = \frac{1}{10} = 0.1 \text{ H}$$

$$C = 10 \mu F$$

9.37

For the op-amp circuit

a

Obtain an expression for $\mathbf{H}(\omega) = \mathbf{V}_0/\mathbf{V}_s$ in standard form

✓ **Answer**

$$\mathbf{H}(\omega) = \frac{R_2 + R_1 - \frac{j}{\omega C}}{R_1 - \frac{j}{\omega C}} = \frac{1 + C(R_2 + R_1)i\omega}{1 + R_1 C i\omega}$$

b


Generate spectral plots for the magnitude and phase of $\mathbf{H}(\omega)$, given that

$$R_1 = 1 \text{ k}\Omega, R_2 = 4 \text{ k}\Omega, C = 1 \mu F$$


✓ **Answer**

$$M(\omega) = \frac{\sqrt{1 + C^2(R_2 + R_1)^2\omega^2}}{\sqrt{1 + R_1^2 C^2\omega^2}}$$
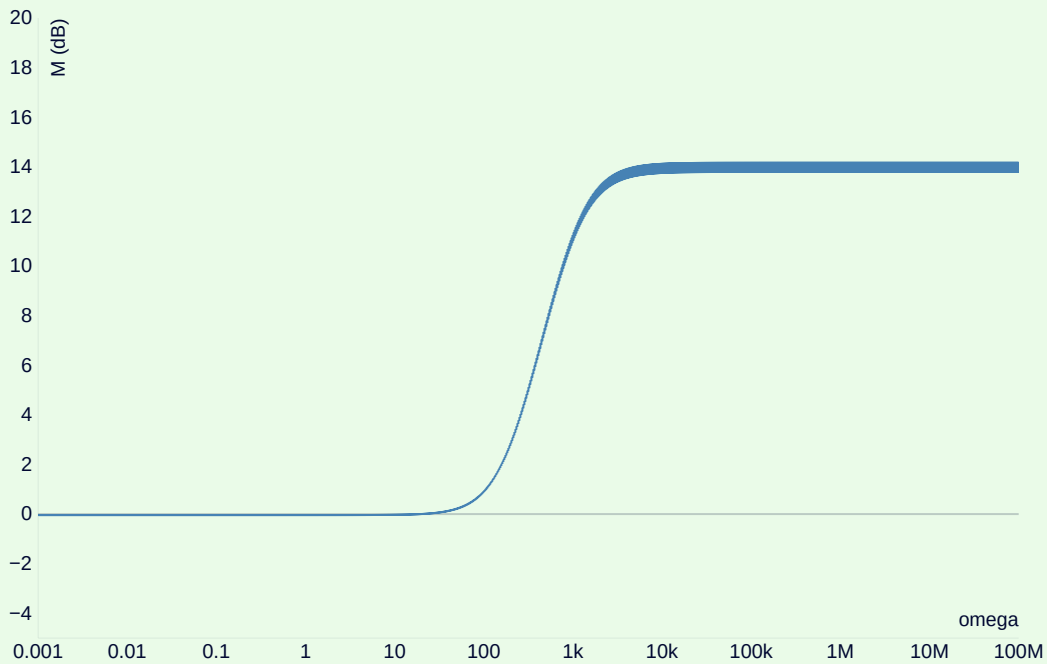
$$M(\omega)[dB] = 10 (\log(1 + C^2(R_1 + R_2)^2\omega^2) - \log(1 + C^2 R_1^2\omega^2))$$


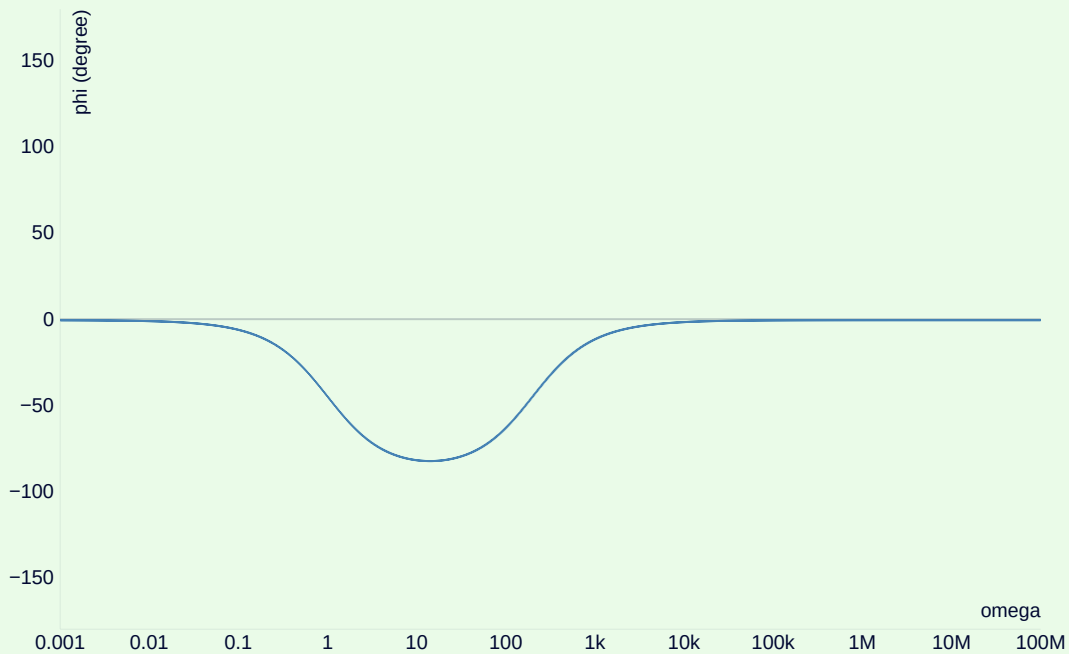
$$\phi(\omega) = \arctan(C(R_2 + R_1)\omega) - \arctan(CR_1\omega)$$



C

What type of filter is it? What is its maximum gain?

✓ **Answer**

This is a high-pass filter, as it boosts the high frequencies while doing nothing with the low frequencies.